

Ultrasonic Distance Measurement Circuit Design

Prepared by Minho Eom

Table of Contents

1. Introduction
2. Design, Simulation & Measurements
3. PCB & Demo photos
4. Issues & Improvements

- 1) Project Overview
- 2) Measurement Principle & Design Specifications
- 3) Block Diagram & Functional Summary (brief)
- 4) Full Schematic

Introduction

1. Project Overview

- **Objective**

- Design an ultrasonic distance measurement circuit (30–100 cm) with 1 cm resolution.

- **Design Tool:**

- Simulation & validation in **OrCAD/Pspice**

- **Applications**

- Automotive **rear parking sensors**, other **proximity detection systems**

2. Measurement Principle & Design Specifications

Measurement Principle


- Distance measured from **TOF (time-of-flight)** of ultrasonic waves
- Formula: $d = \frac{c \times \Delta t}{2}$, with $c \approx 340 \text{ m/s}$ (at room temperature)
- Example: 1 m round trip $\approx$ **5.8 ms**
- Measure Tx–Rx delay $\rightarrow$ distance output

Design Specifications

- transmit frequency: **40 kHz ultrasonic burst**
- Burst period: **~65 ms** (~15 Hz)
- Counter clock: **17.2 kHz** ($\approx$ 100 counts per 1 m round trip; 1cm resolution)
- Supply: **12 V DC**
- Display: **3-digit 7-Segment**


Introduction

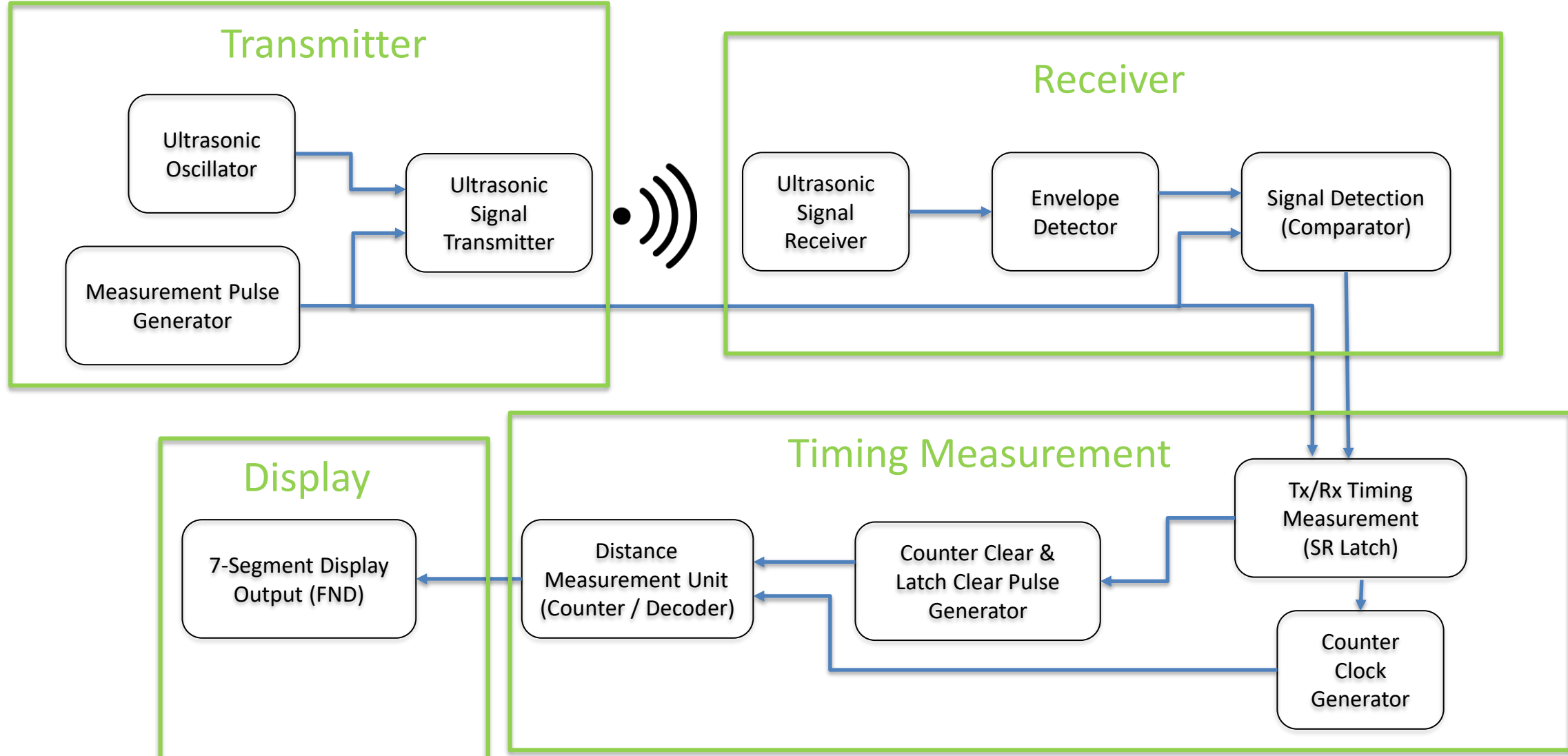3. Block Diagram & Functional Summary (brief)




Introduction

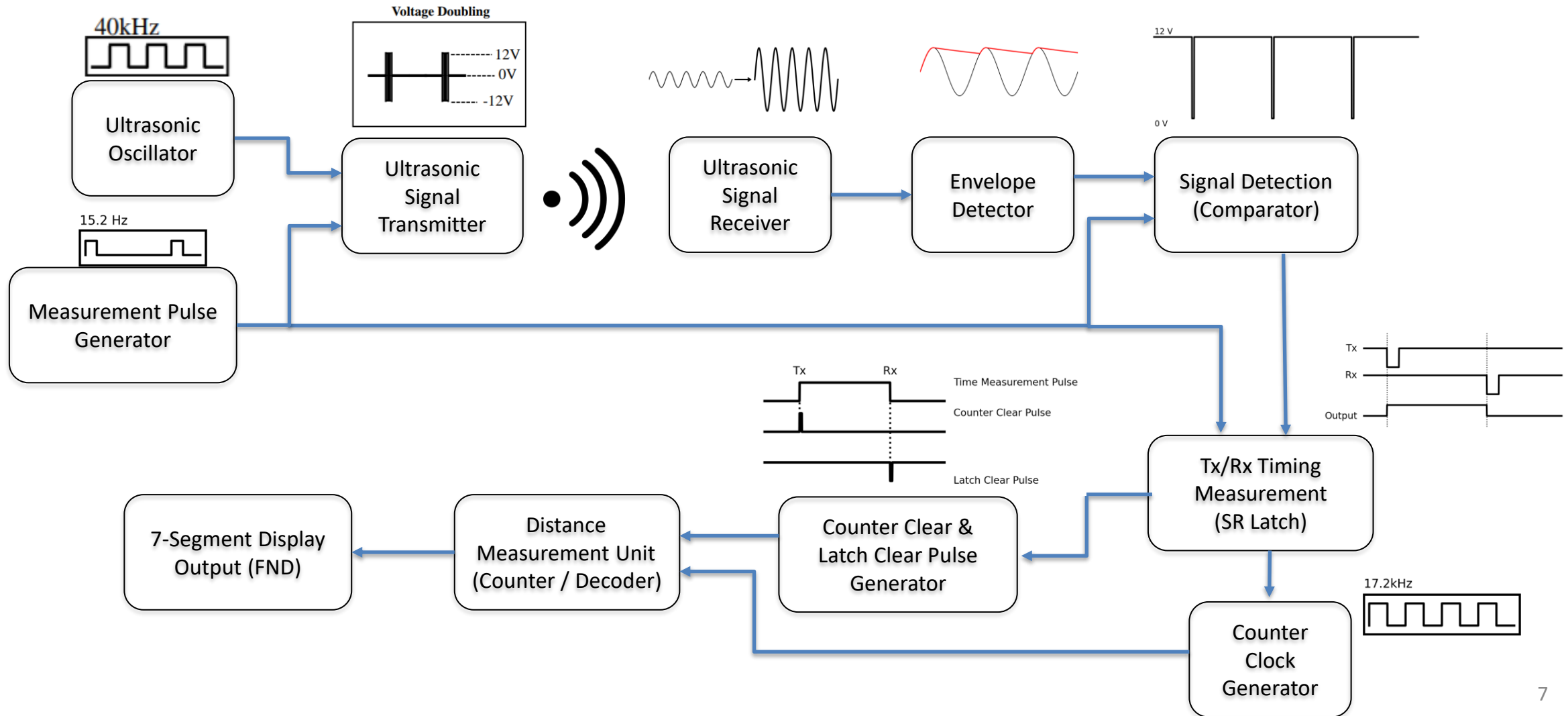3. Block Diagram & Functional Summary (brief)



Introduction

4. Overall Circuit Schematic

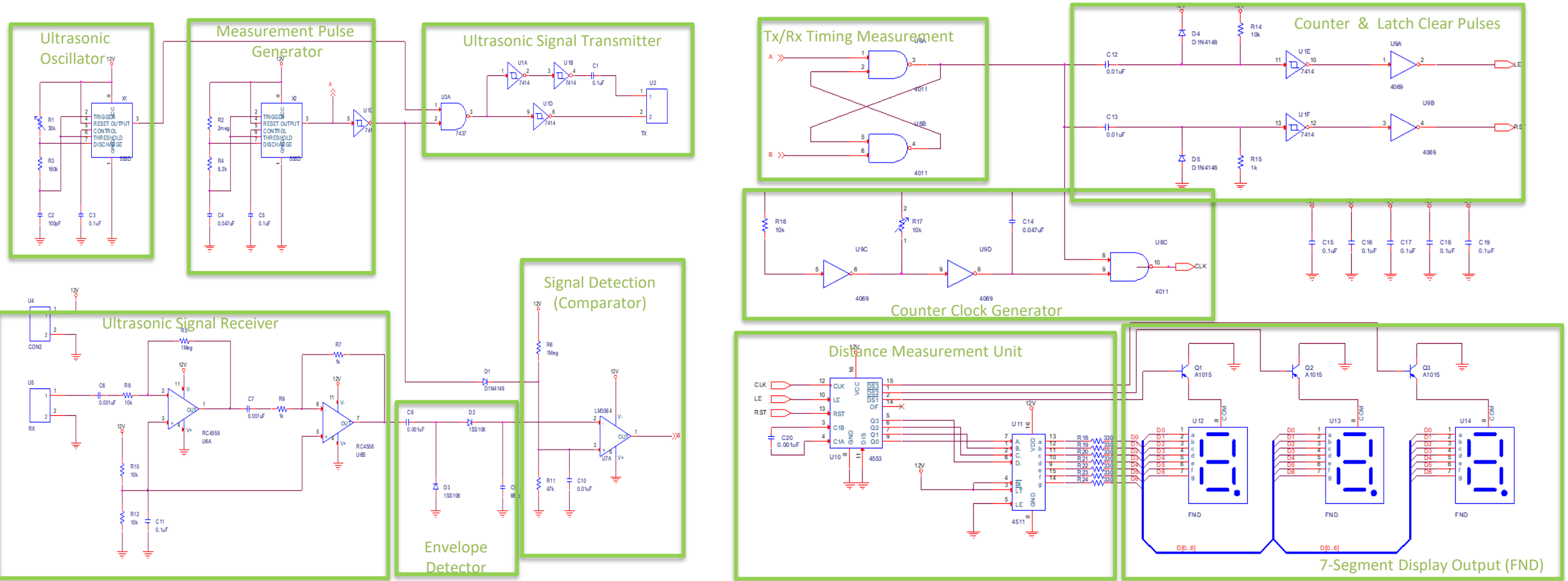

Introduction

5. Bill of Materials (BOM)

No.	Part Name	Spec	Qty
1	Chip IC NE555 (SMD)	–	1
2	IC NE555	–	1
3	IC 4584	–	1
4	IC 4011	–	1
5	IC RC4558	–	1
6	IC LM358	–	1
7	IC 4069	–	1
8	IC 4553	–	1
9	IC 4511	–	1
10	IC Socket 8-Pin	–	3
11	IC Socket 14-Pin	–	3
12	IC Socket 16-Pin	–	2
13	Transistor A1015	–	3
14	FND 500 (7-Segment)	–	3
15	Ultrasonic Sensor TX	SE-400ST160	1
16	Ultrasonic Sensor RX	SE-400SR160	1
17	Diode 1SS106	–	2
18	Diode 1N4148	–	3
19	Connector (2P, Green)	–	1
20	Bare PCB	–	1
21	Resistor	150 k Ω , 1/4 W, 1%	1

No.	Part Name	Spec	Qty
20	Bare PCB	–	1
21	Resistor	150 k Ω , 1/4 W, 1%	1
22	Resistor	10 k Ω , 1/4 W, 1%	8
23	Resistor	2 M Ω , 1/4 W, 1%	1
24	Resistor	8.2 k Ω , 1/4 W, 1%	1
25	Resistor	1 M Ω , 1/4 W, 1%	2
26	Resistor	47 k Ω , 1/4 W, 1%	1
27	Resistor	1 k Ω , 1/4 W, 1%	2
28	Chip Resistor (SMD)	330 Ω (2012)	7
29	Mylar Capacitor	0.047 μ F	1
30	Ceramic Capacitor	680 pF	1
31	Ceramic Capacitor	100 pF	1
32	Ceramic Capacitor	0.1 μ F	9
33	Ceramic Capacitor	0.01 μ F	3
34	Ceramic Capacitor	0.001 μ F	4
35	Ceramic Capacitor	0.0047 μ F	1
36	Trimmer Resistor	47 k Ω	1
37	Trimmer Resistor	10 k Ω	1

Introduction

- 1) Ultrasonic Oscillator
- 2) Measurement Pulse Generator
- 3) Ultrasonic Signal Transmitter
- 4) Ultrasonic Signal Receiver
- 5) Envelope Detector
- 6) Signal Detection (Comparator)
- 7) Tx/Rx Timing Measurement (SR Latch)
- 8) Counter Clock Generator
- 9) Counter Clear & Latch Clear Pulse Generator
- 10) Time Measurement Unit (Counter / Decoder) & 7-Segment Display Output (FND)

1. Ultrasonic Oscillator

Block Purpose & Function

1. Generate a 40 kHz ultrasonic carrier (square wave) to drive the TX stage.

Design, Simulation & Measurements


1. Ultrasonic Oscillator



Specification

400ST160	Transmitter
400SR160	Receiver
Center Frequency	40.0±1.0KHz
Bandwidth (-6dB)	400ST160 2.0KHz 400SR160 2.5KHz
Transmitting Sound Pressure Level at 40.0KHz, 0dB re 0.0002μbar per 10Vrms at 30cm	120dB min.
Receiving Sensitivity at 40.0KHz 0dB = 1 volt/μbar	-61dB min.
Capacitance at 1KHz ±20%	2400 pF
Max. Driving Voltage (cont.)	20Vrms
Total Beam Angle	-6dB 55° typical
Operation Temperature	-30 to 70°C
Storage Temperature	-40 to 80°C

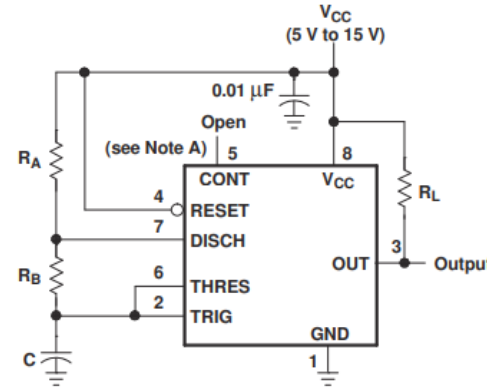
All specification taken typical at 25°C
Closer frequency tolerance can be supplied upon request.



$$t_H \cong 0.693 \times (R_A + R_B) \times C$$

$$t_L \cong 0.693 \times R_B \times C$$
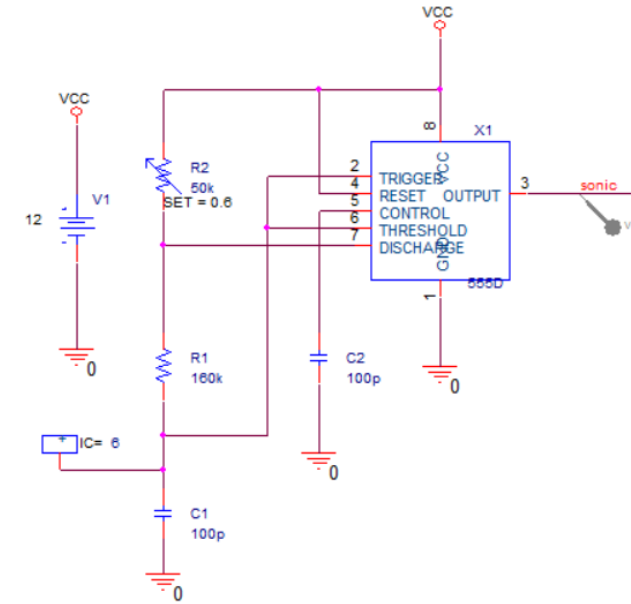
$$f = \frac{1}{T} \cong \frac{1.44}{(R_A + 2R_B) \times C}$$







- **Resonant Frequency:** SE-400ST160 requires **40 kHz** for maximum output.
- **Oscillator Design:** Target frequency set to **40 kHz**.
- **NE555 Formula:**

$$F = \frac{1.44}{(R_A + 2R_B) \times C} [\text{Hz}],$$

- **Implementation:** Select proper **R1**, **R2**, **C1** to achieve 40 kHz.

Design, Simulation & Measurements



1. Ultrasonic Oscillator

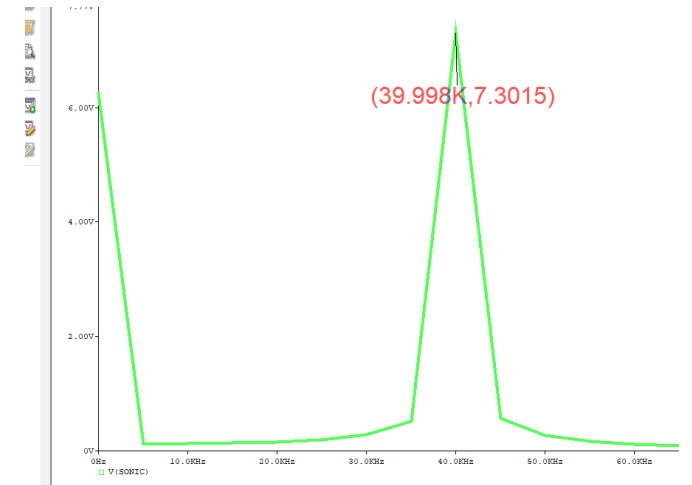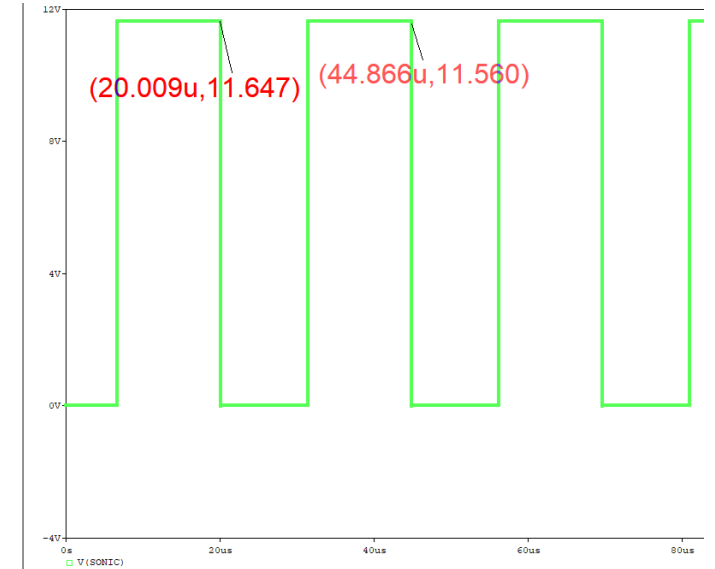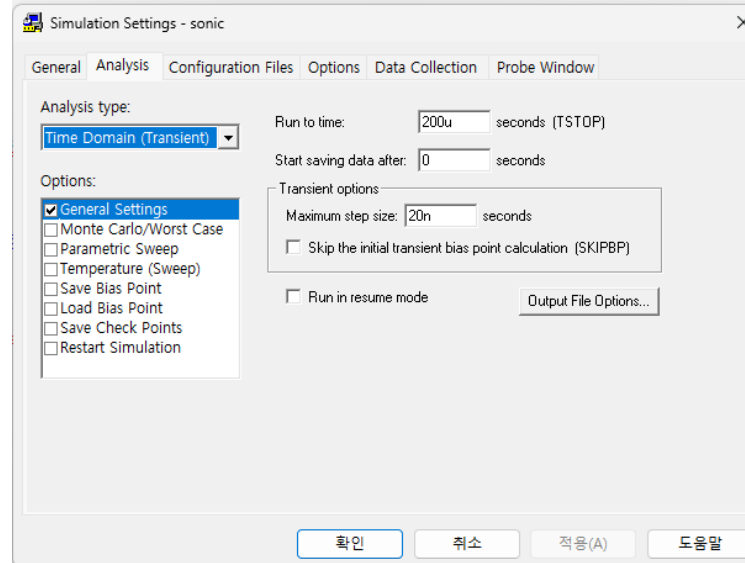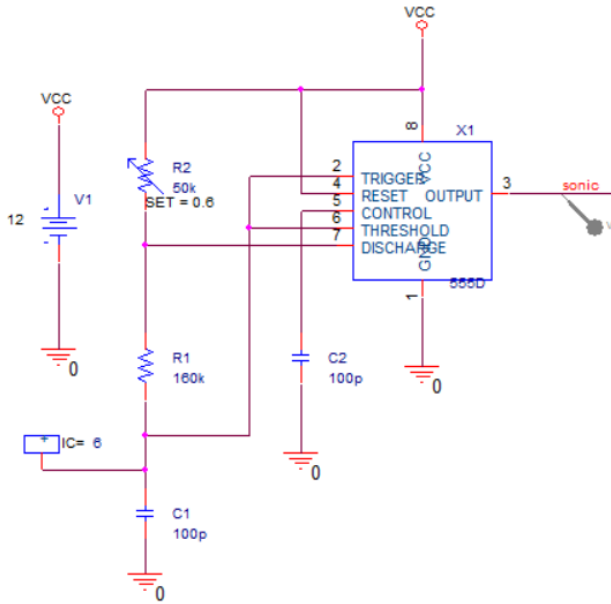

$$\begin{aligned}
 (R1 &= 30 \text{ k}\Omega \quad R2 = 160 \text{ k}\Omega \quad C1 = 100 \text{ pF}) \\
 t_L &= 0.69 \times 160 \times 10^3 \times 100 \times 10^{-12} \approx 11 \mu\text{sec} \\
 t_H &= 0.69 \times (160+30) \times 10^3 \times 100 \times 10^{-12} \approx 13 \mu\text{sec} \\
 f &= \frac{1.44}{\{(30 + 2 \times 160) \times 10^3\} \times 100 \times 10^{-12}} \approx 41.1 \text{ kHz}
 \end{aligned}$$

Design, Simulation & Measurements

1. Ultrasonic Oscillator

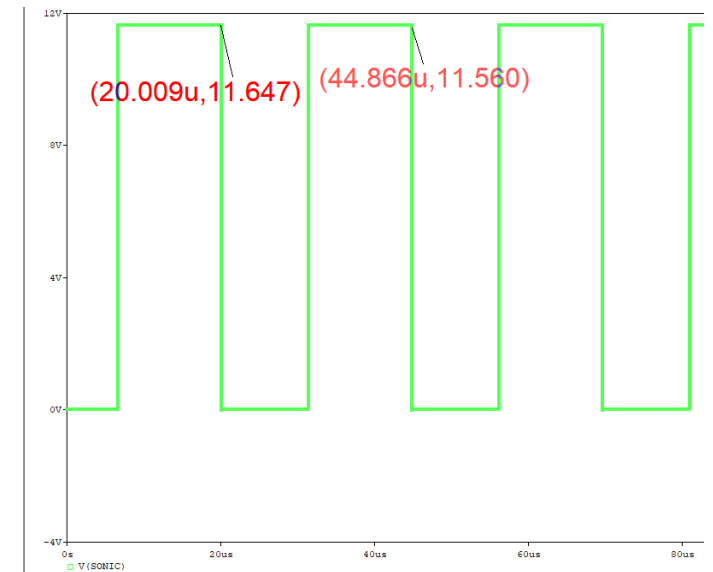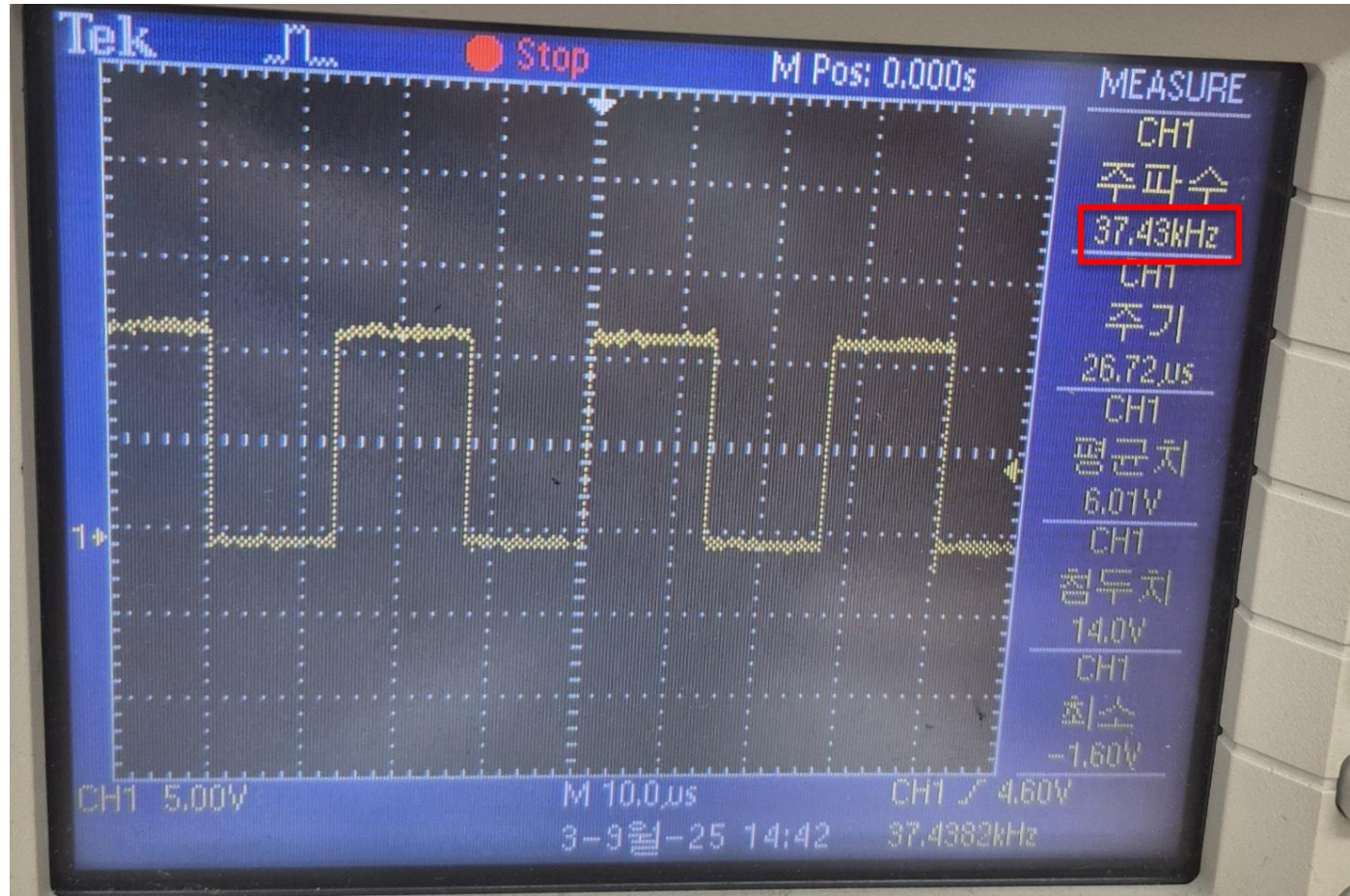


2. Measurement Pulse Generator

Block Purpose & Function

1. Generate timing pulses for ultrasonic burst transmission
2. Produce one pulse approximately every 65 ms (≈ 15.2 Hz)

Design, Simulation & Measurements




2. Measurement Pulse Generator

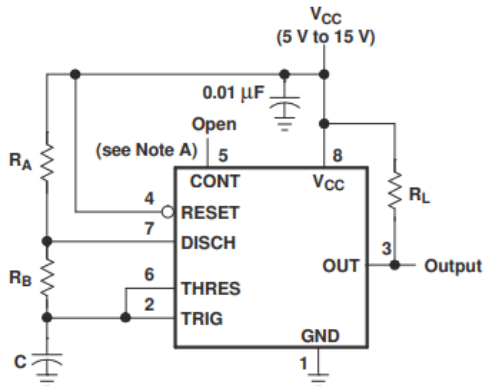

$$t_H \cong 0.693 \times (R_A + R_B) \times C$$

$$t_L \cong 0.693 \times R_B \times C$$
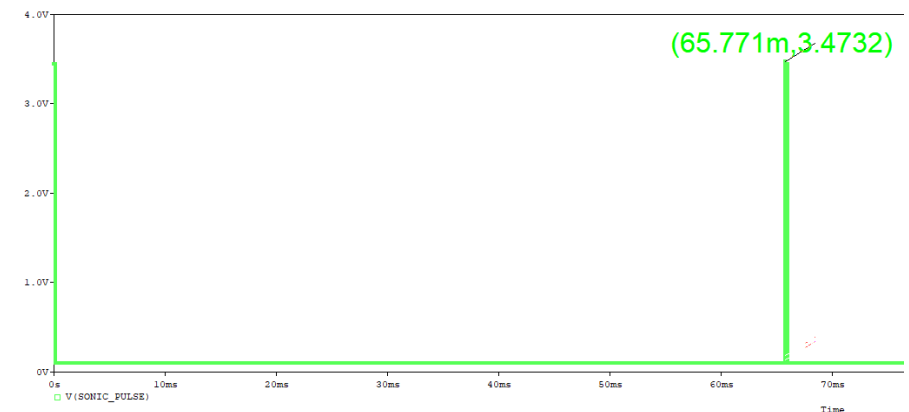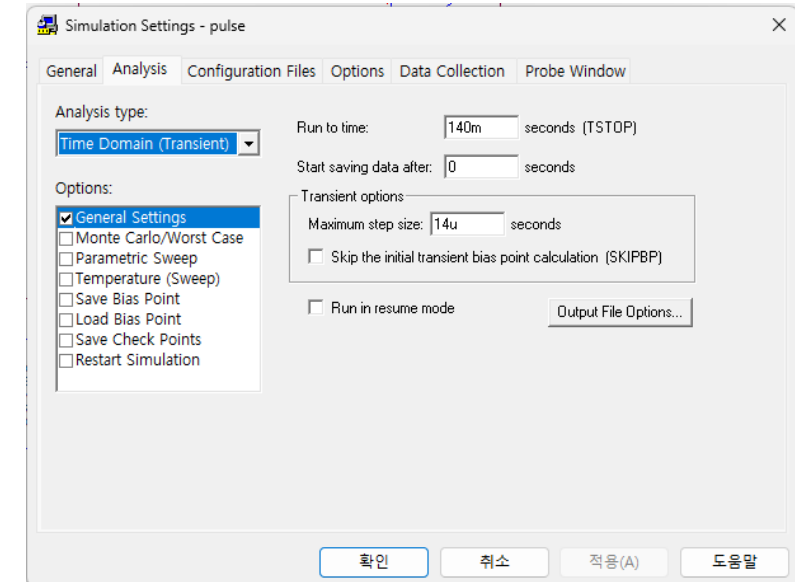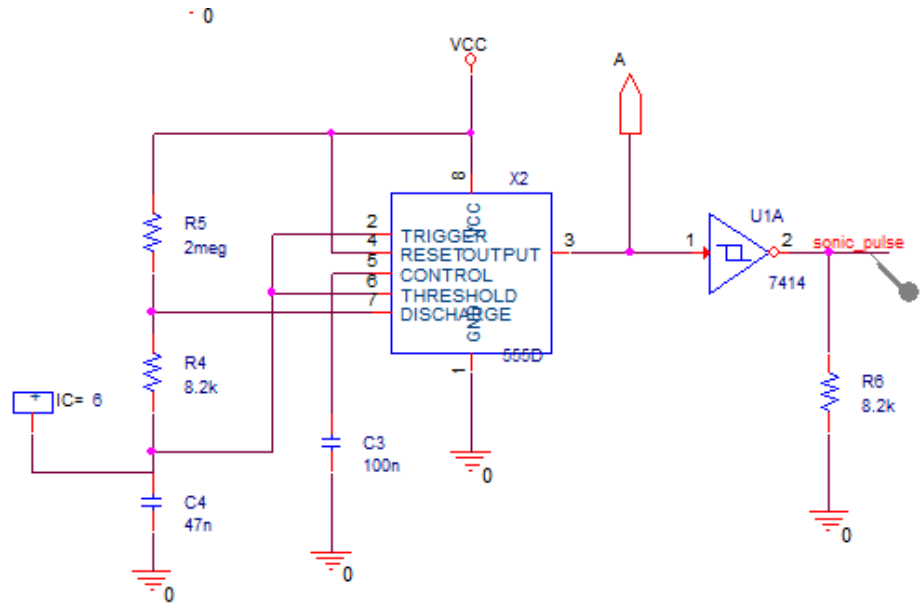
$$f = \frac{1}{T} \cong \frac{1.44}{(R_A + 2R_B) \times C}$$




$$t_H = 0.69 \times (2 \times 10^6 + 8200) \times 47 \times 10^{-9} \approx 65.125 \text{ msec}$$

$$t_L = 0.69 \times 2 \times 10^6 \times 47 \times 10^{-9} \approx 265.92 \text{ usec}$$

$$f = \frac{1.44}{\{(2 \times 10^6 + 2 \times 8200) \times 47 \times 10^{-9}\}} \approx 15.19 \text{ Hz}$$

Design, Simulation & Measurements

2. Measurement Pulse Generator

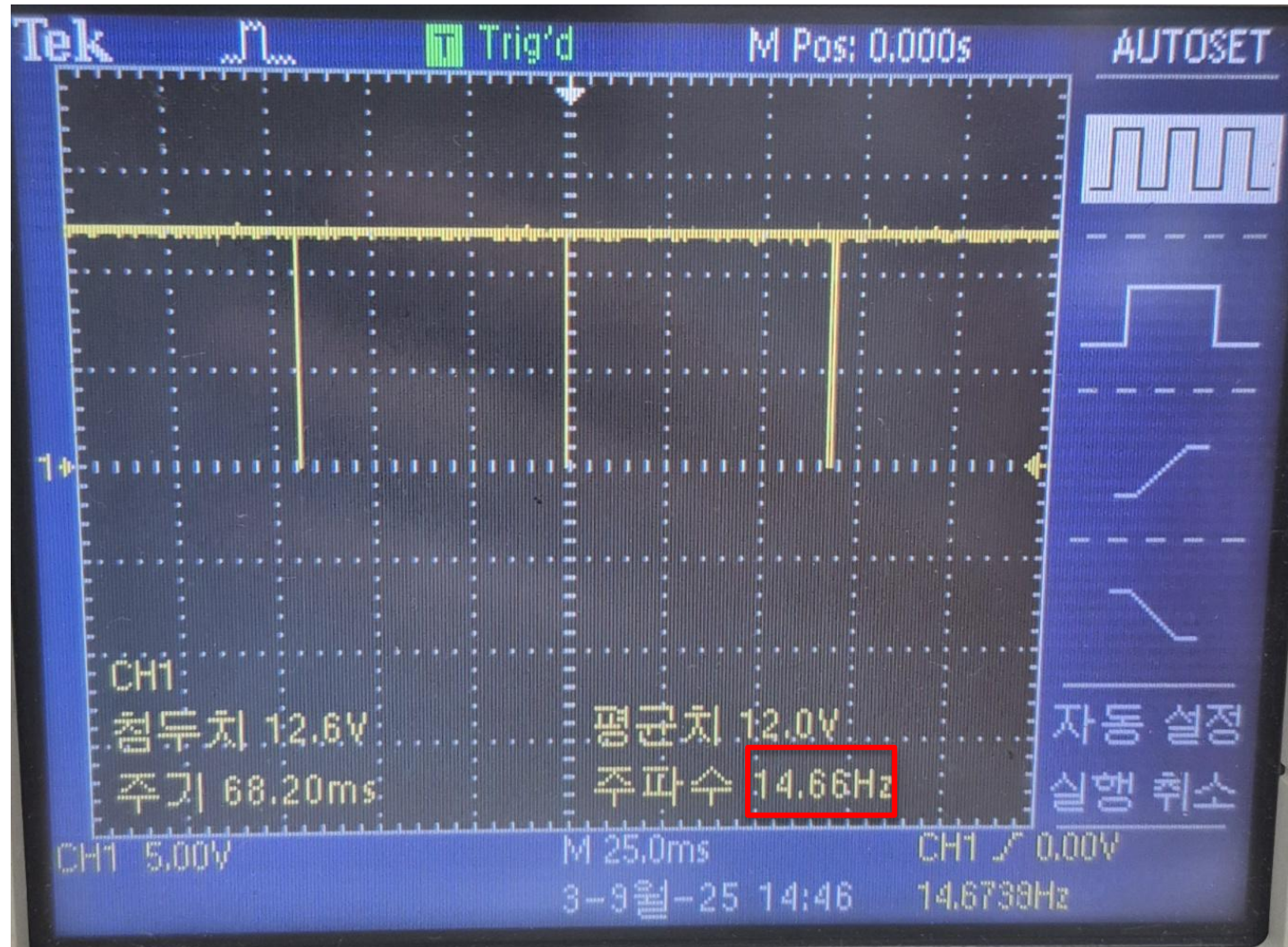


3. Ultrasonic Signal Transmitter

Block Purpose & Function

1. Transmit 40 kHz ultrasonic bursts according to timing pulses
2. Use NAND gate masking and buffer/voltage doubler for stronger drive




Design, Simulation & Measurements

3. Ultrasonic Signal Transmitter

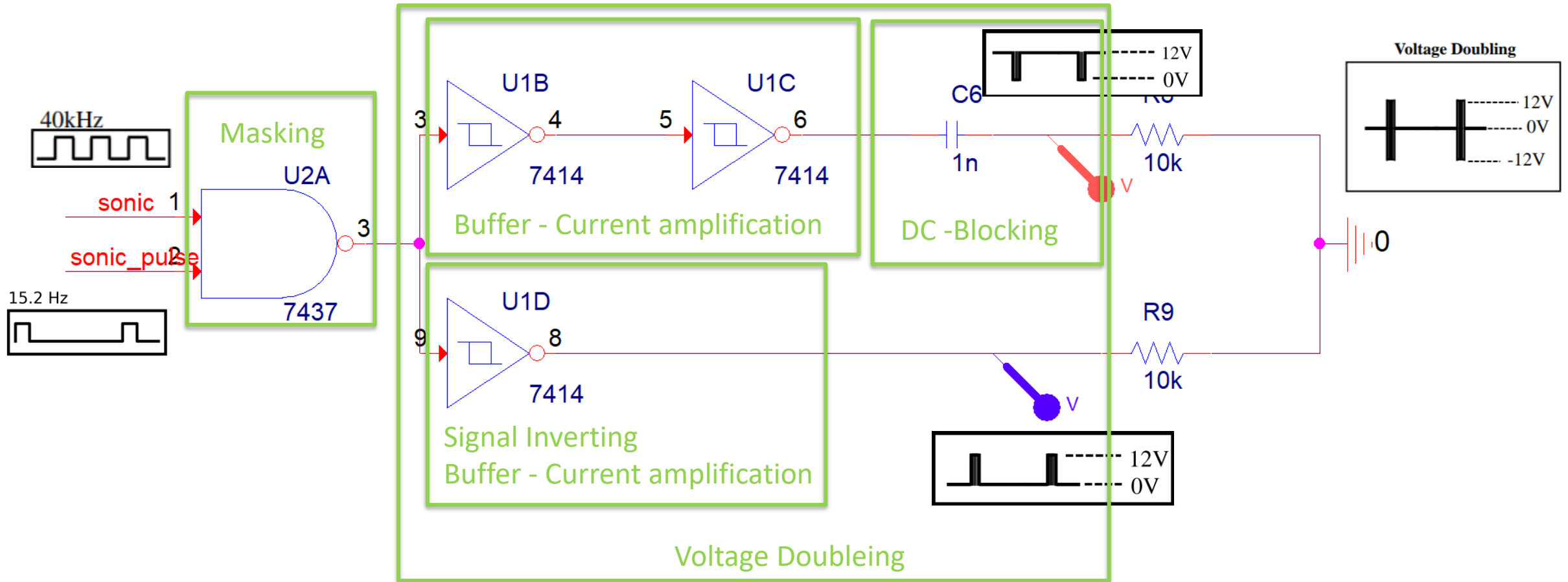


Design, Simulation & Measurements

3. Ultrasonic Signal Transmitter

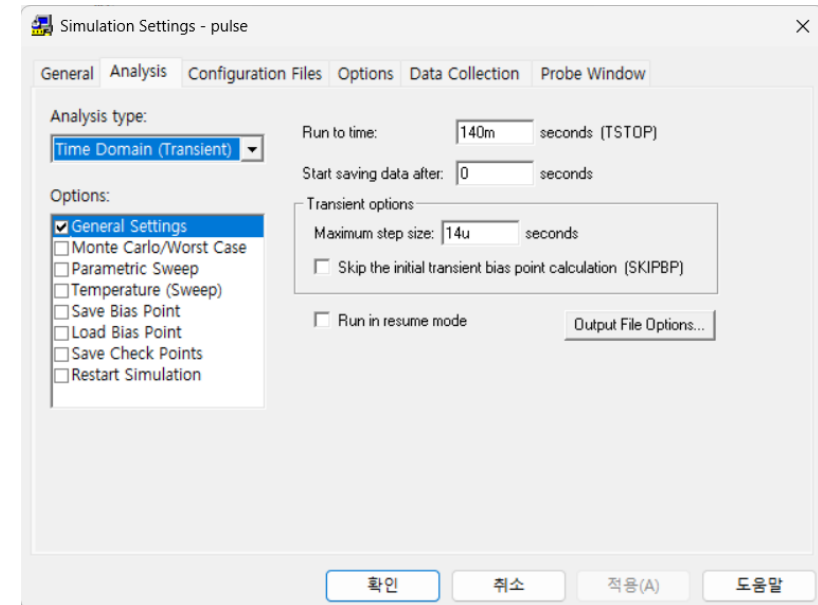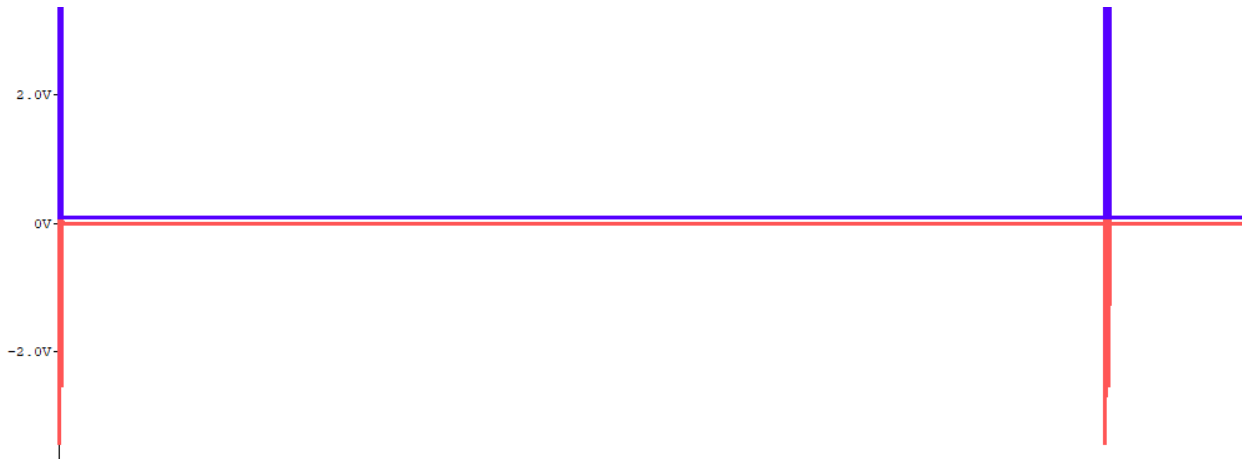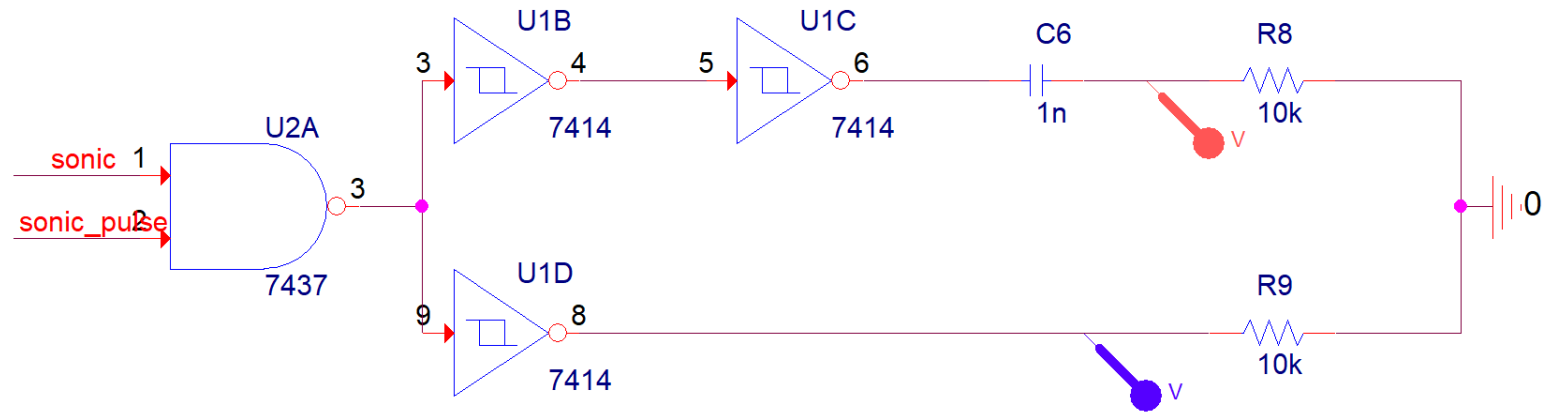

3. Ultrasonic Signal Transmitter

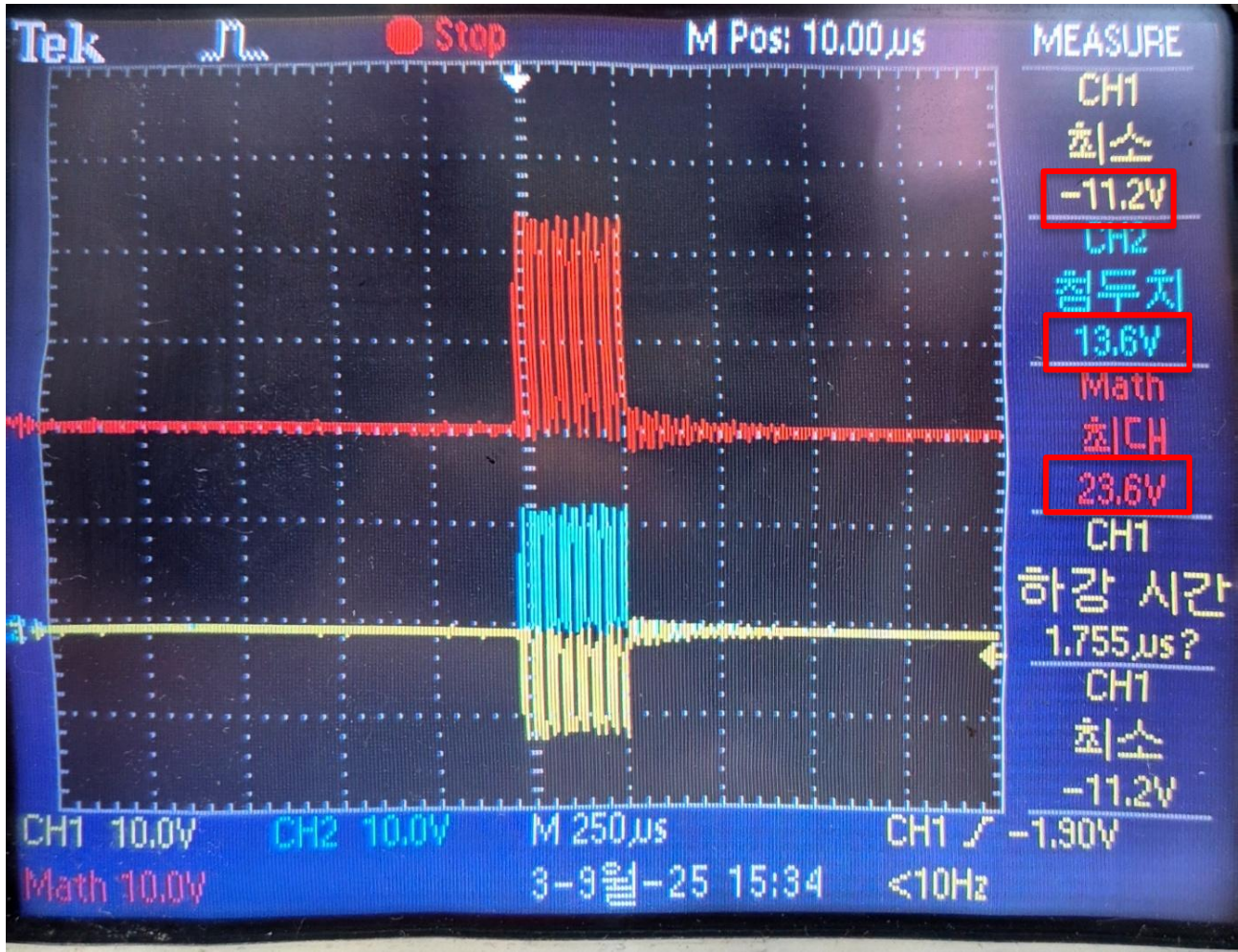



4. Ultrasonic Signal Receiver

Block Purpose & Function


1. Receive reflected 40 kHz ultrasonic signals
2. Amplify weak received signals using a two-stage OP-Amp

Design, Simulation & Measurements

4. Ultrasonic Signal Receiver

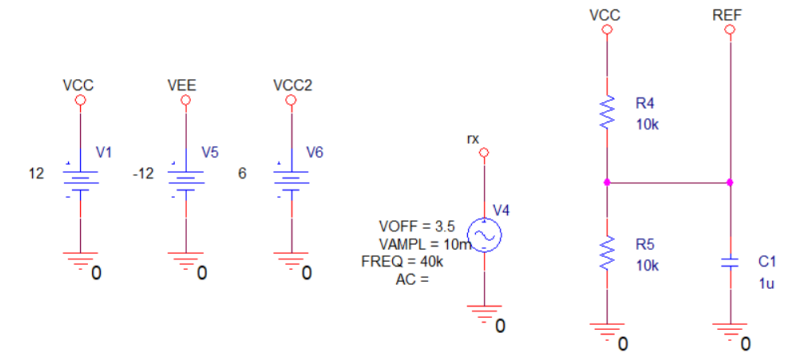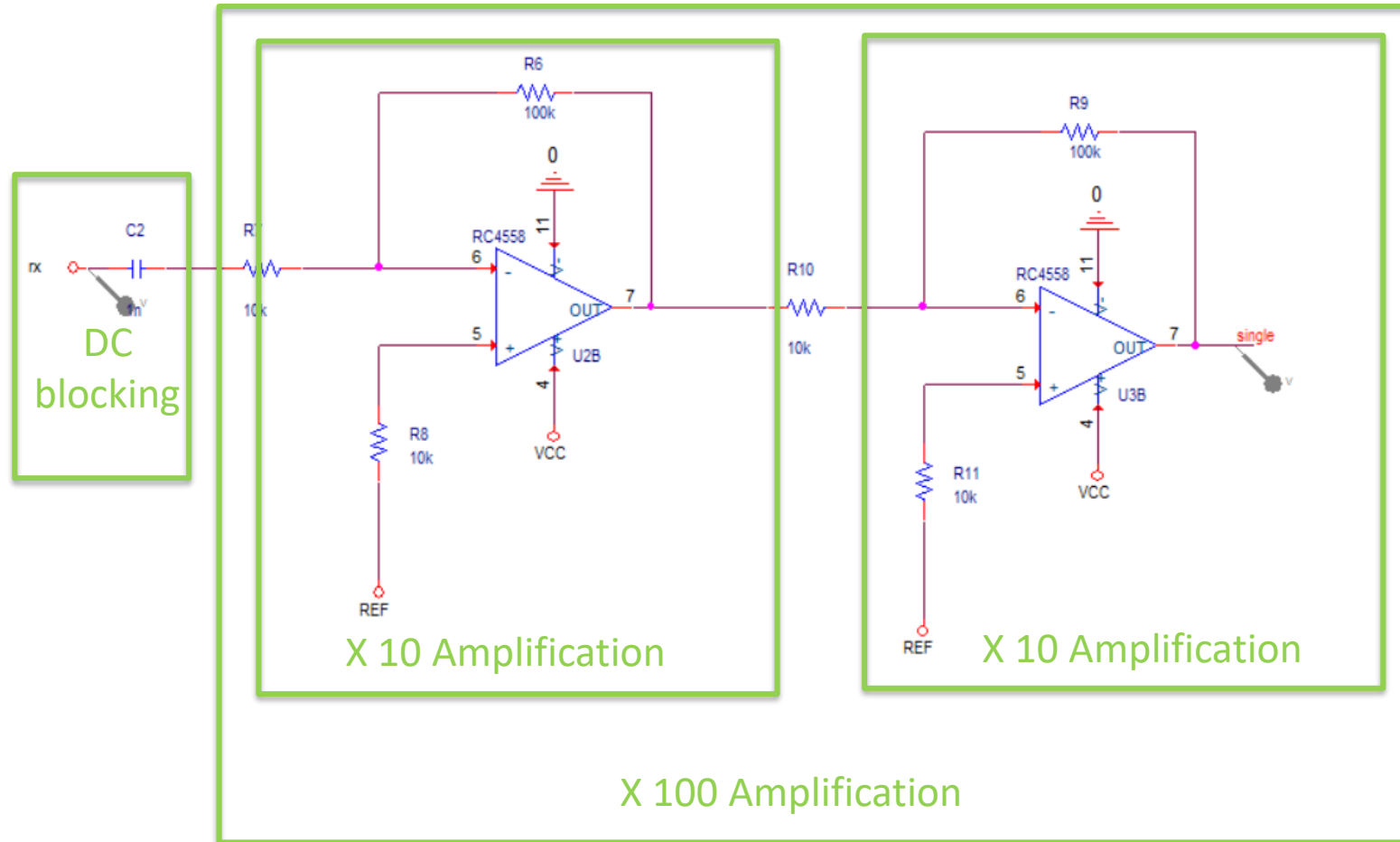

4. Ultrasonic Signal Receiver

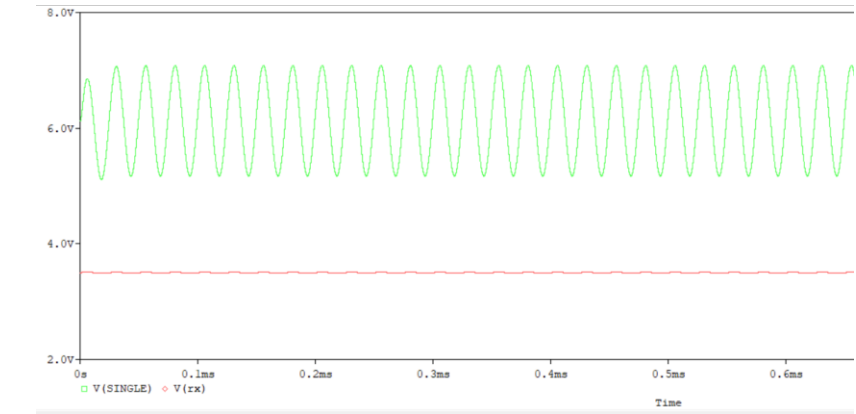





5. Envelope Detector

Block Purpose & Function

1. Rectify the amplified signal using diodes
2. Smooth the waveform to extract the envelope (closer to DC)



Design, Simulation & Measurements

5. Envelope Detector

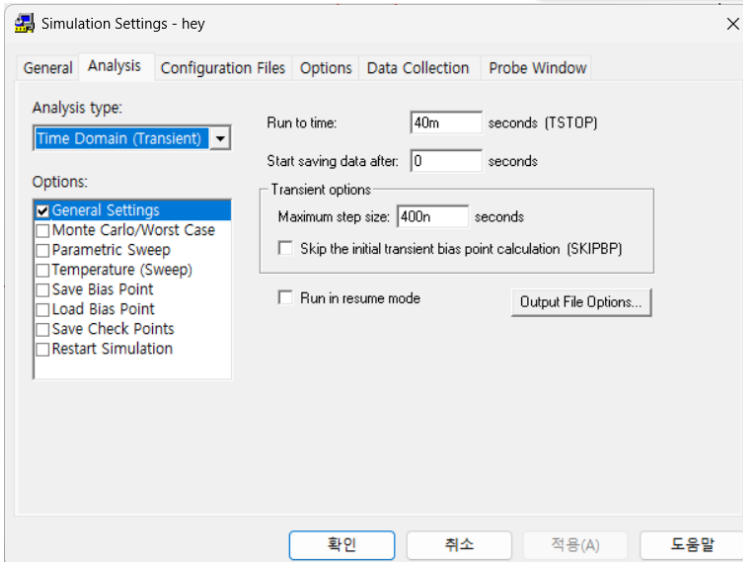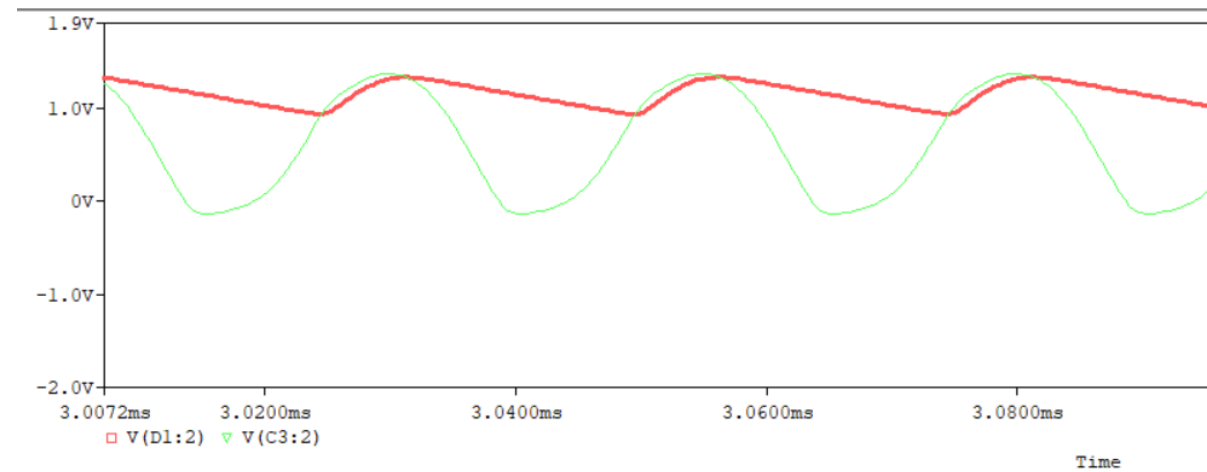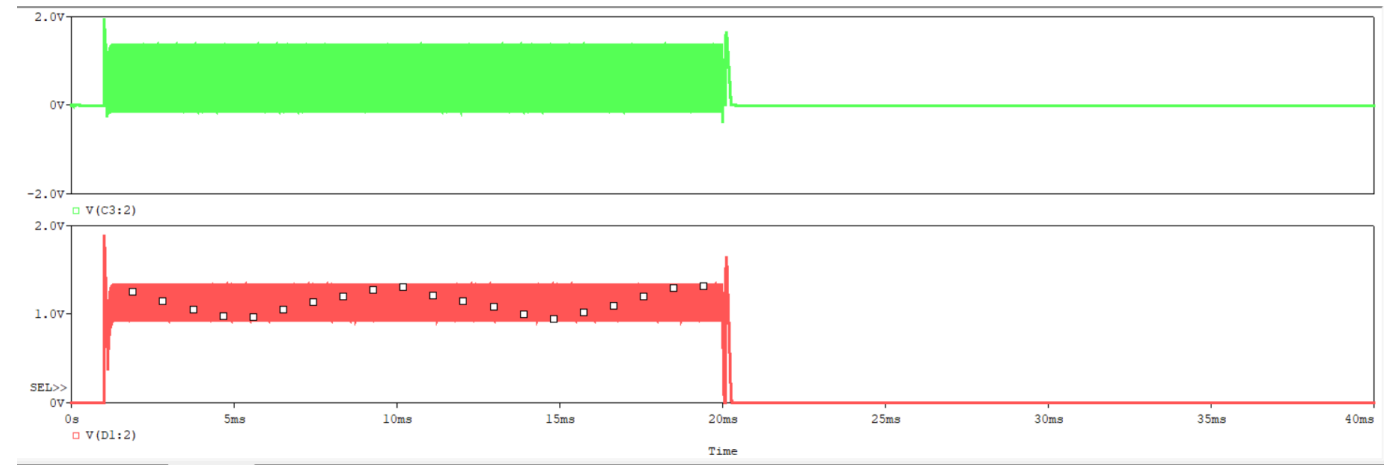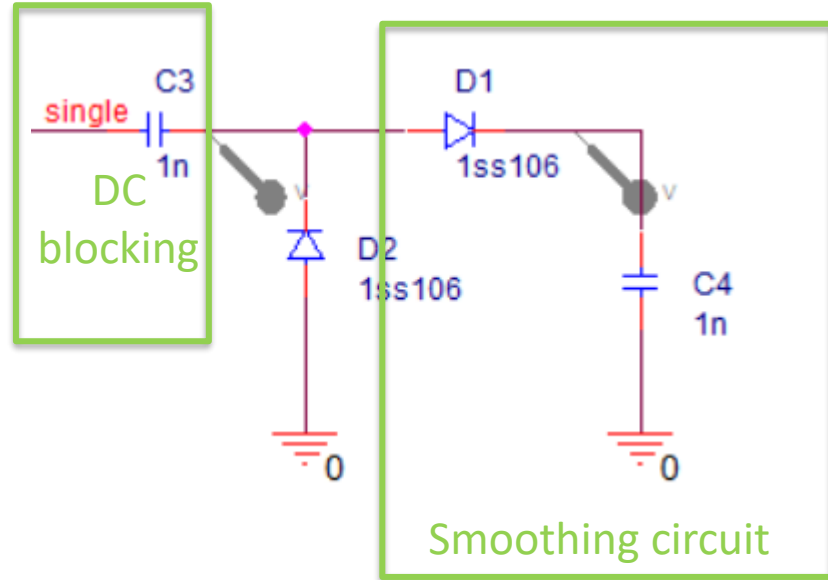

Design, Simulation & Measurements

5. Envelope Detector

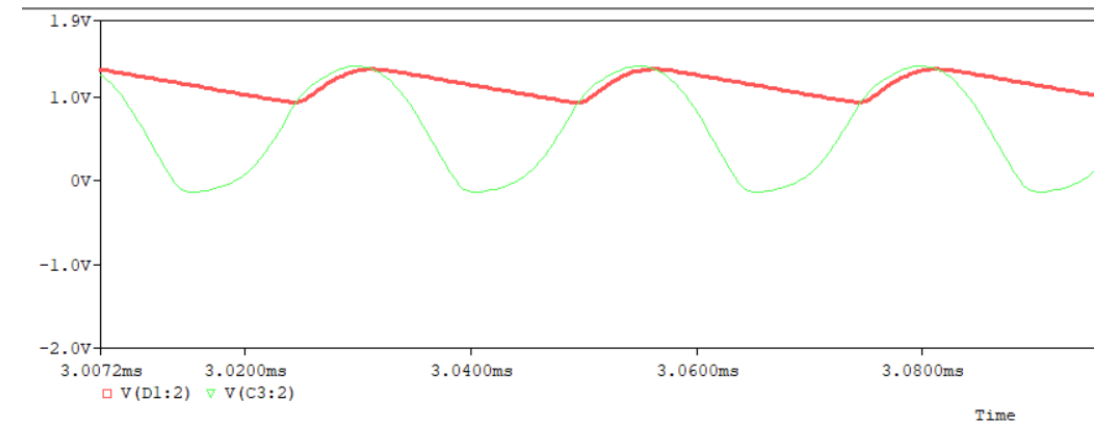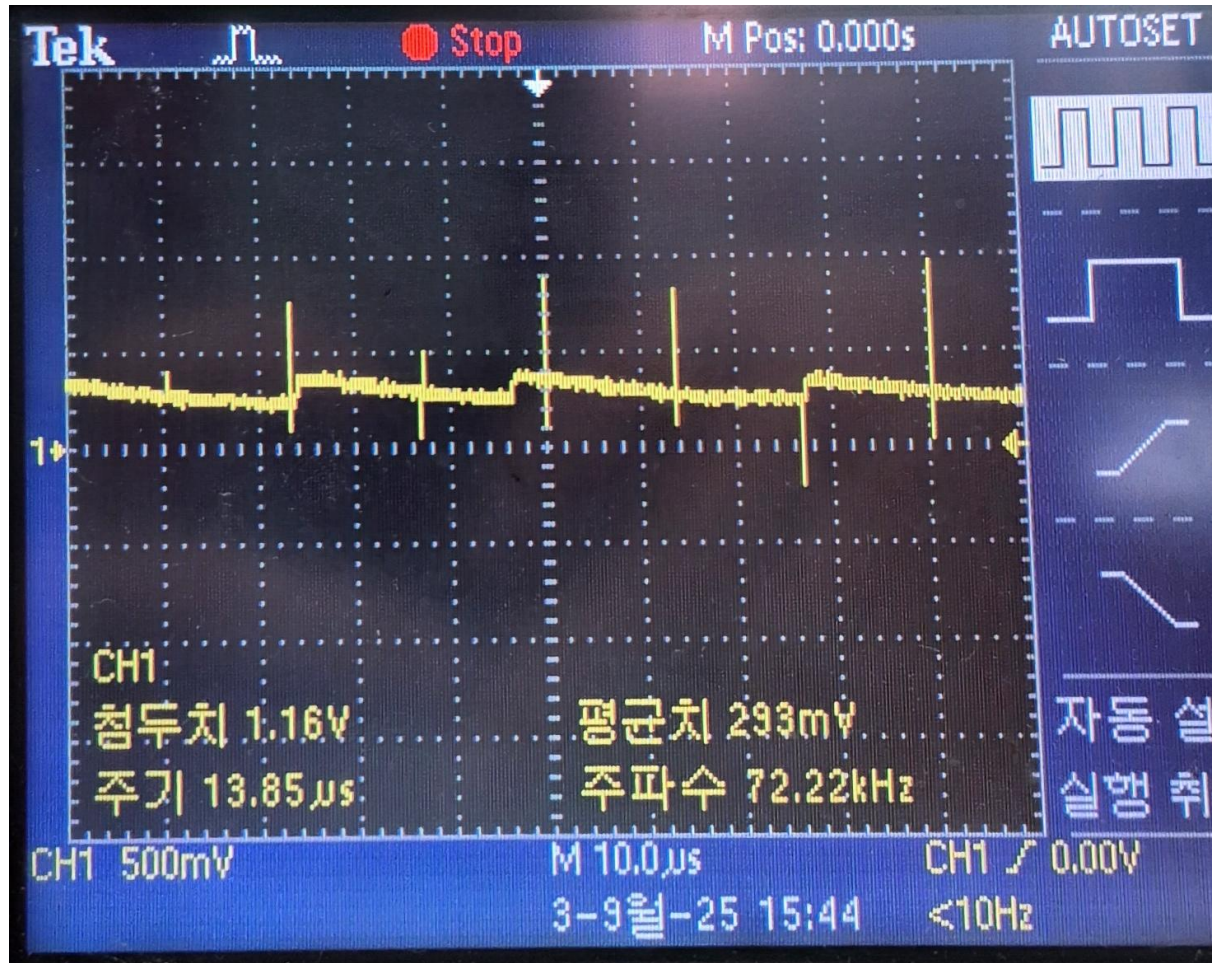


6. Signal Detection (Comparator)

Block Purpose & Function

1. Detect valid received signals using an OP-Amp comparator (active-low output)
2. Block unwanted signals with diode feedback
3. Suppress noise by allowing only signals above $\sim 0.54\text{ V}$



Design, Simulation & Measurements

6. Signal Detection (Comparator)

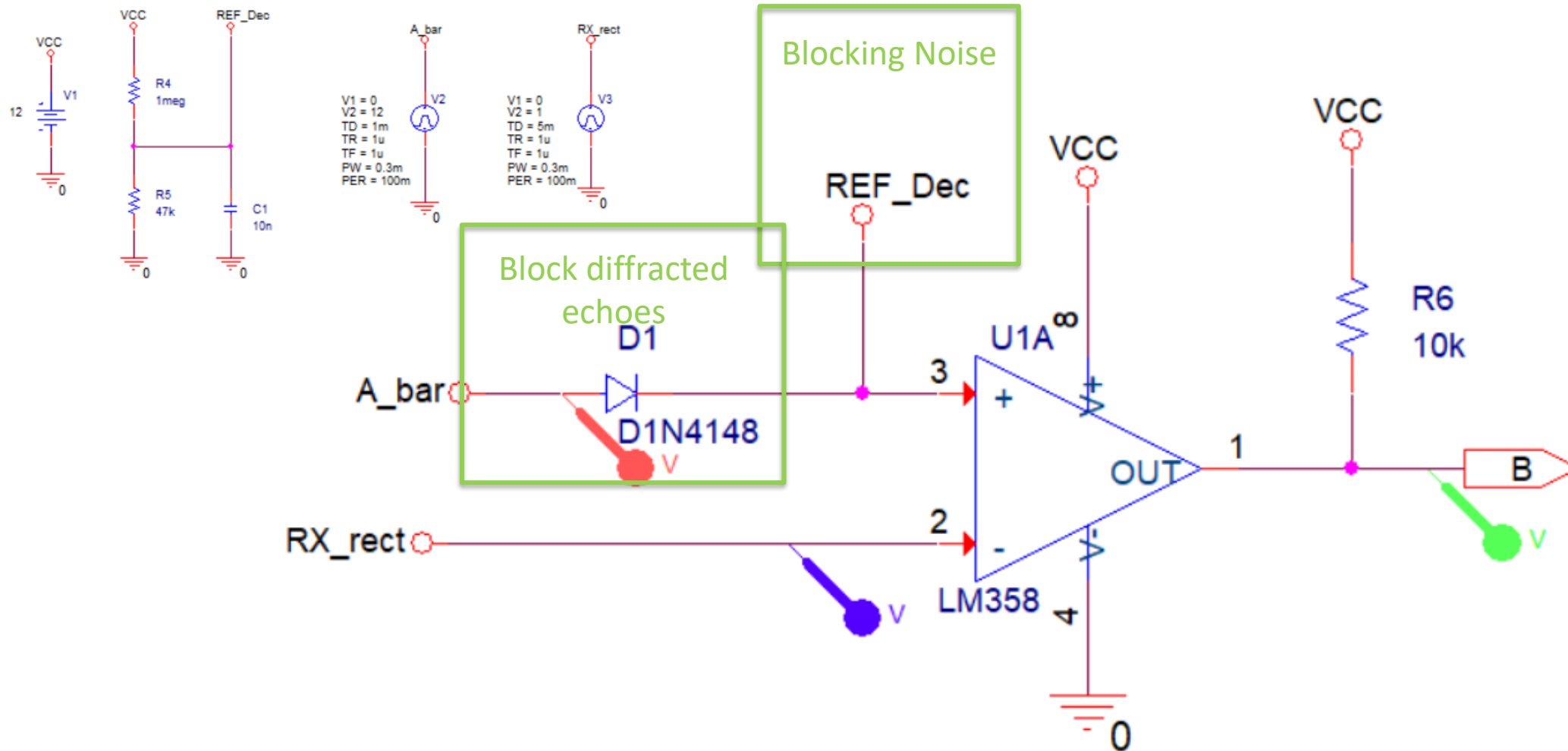

Design, Simulation & Measurements

6. Signal Detection (Comparator)

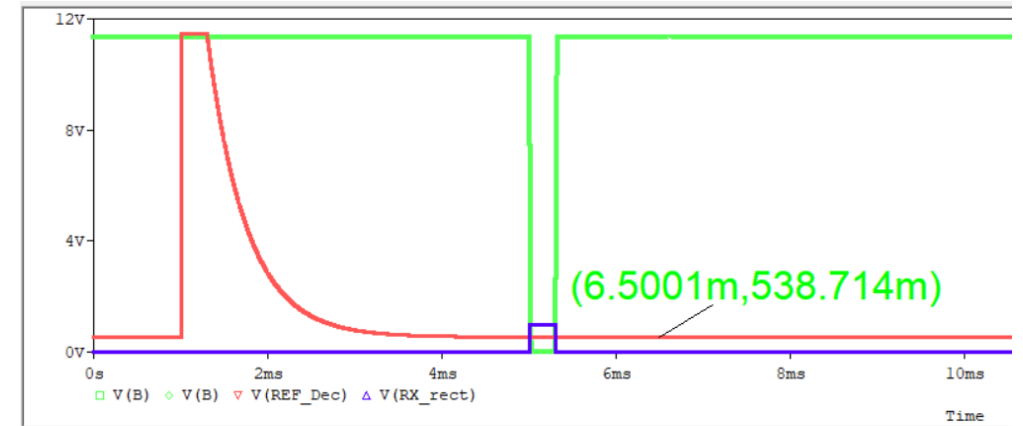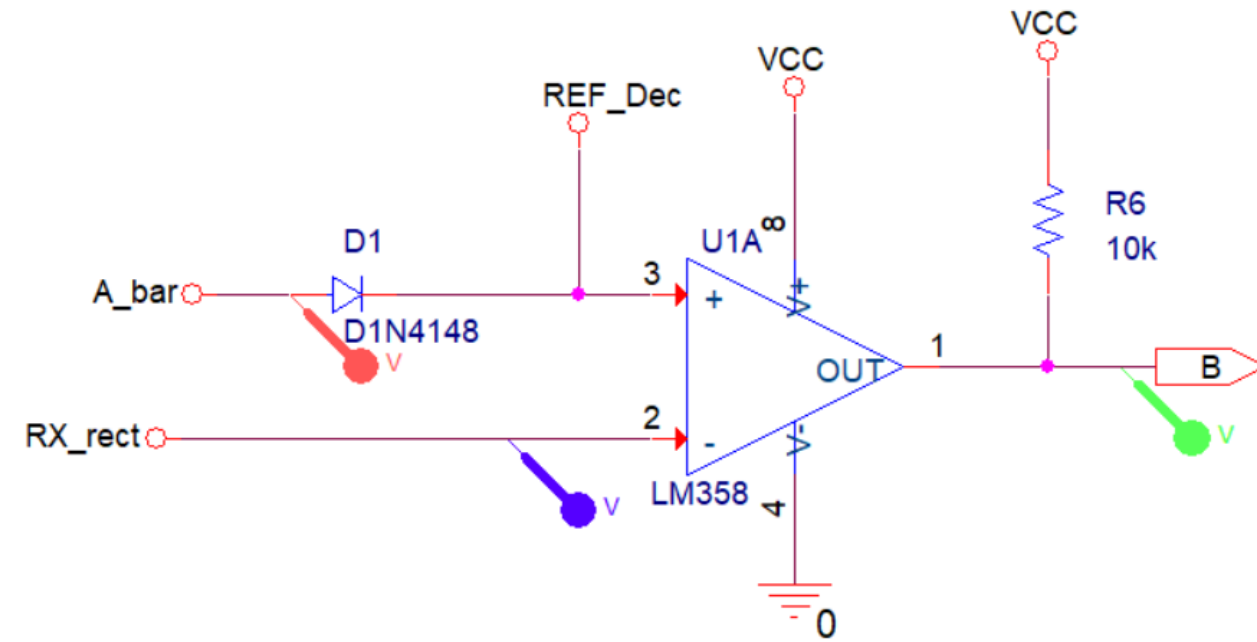

OP-Amp Comparator

- Slow but stable operation

1. $V_+ > V_- \rightarrow \text{Output} = V_{CC}$, $V_+ < V_- \rightarrow \text{Output} = \text{GND}$

2. Signal detection $\rightarrow$ Output GND (**Active Low**)

Vref

- Noise rejection

$\rightarrow$ Detect only signals above $\sim 0.54 \text{ V}$

D1 Diode



- Blocking diffracted echoes

1. Timing pulse $\rightarrow$ applied to V_+ input

2. Capacitor delay $\rightarrow$ detection time is delayed

3. Ignore signals arriving during this time (diffracted echoes)

6. Signal Detection (Comparator)

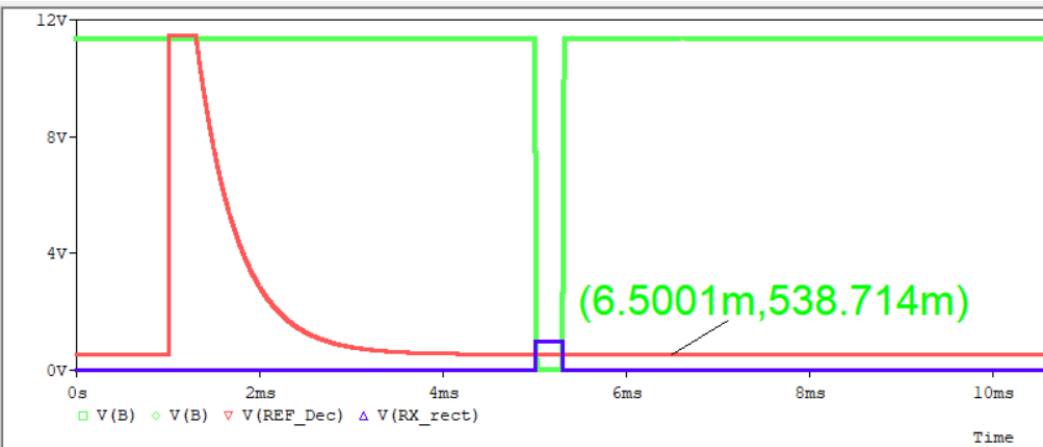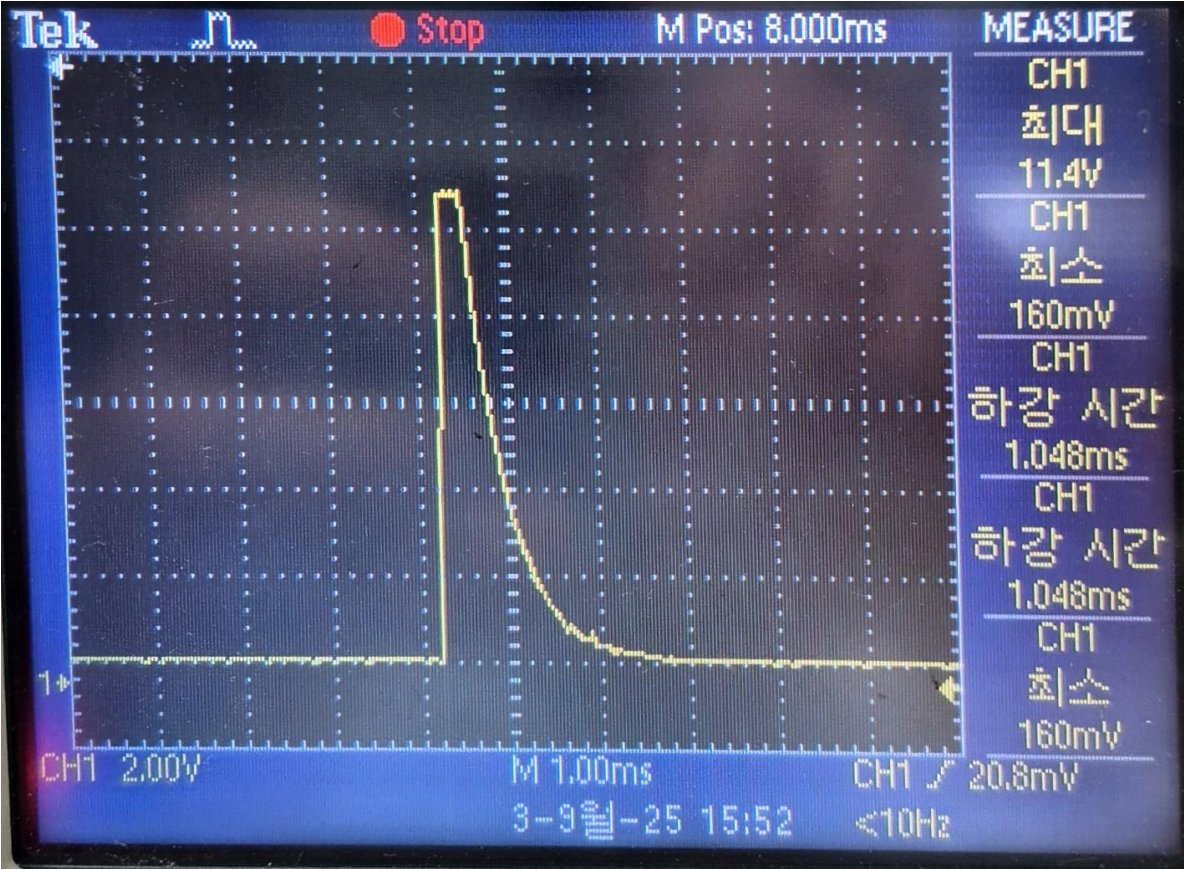


7. Tx/Rx Timing Measurement (SR Latch)

Block Purpose & Function


1. Measure the time difference between transmission and reception
2. Use SR latch to generate a gate signal for the counter

7. Tx/Rx Timing Measurement (SR Latch)

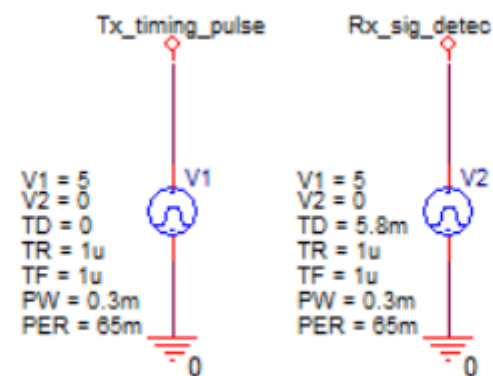




S	R	Q	Q_bar	Operation
1	1	Q	Q_bar	Hold
0	1	1	0	Set
1	0	0	1	Reset
0	0	Invalid	Invalid	Forbidden

<SR Latch Truth Table>

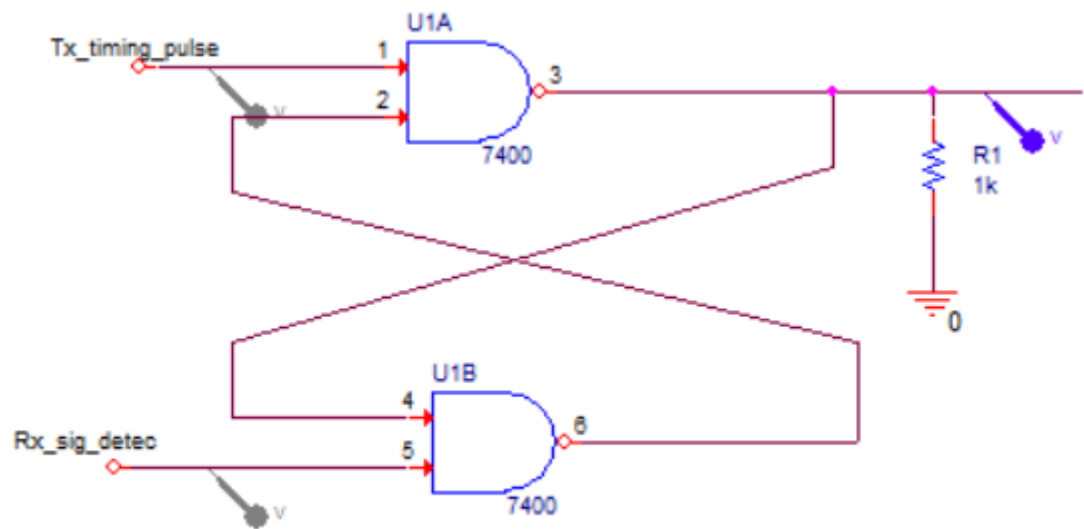

Design, Simulation & Measurements

7. Tx/Rx Timing Measurement (SR Latch)

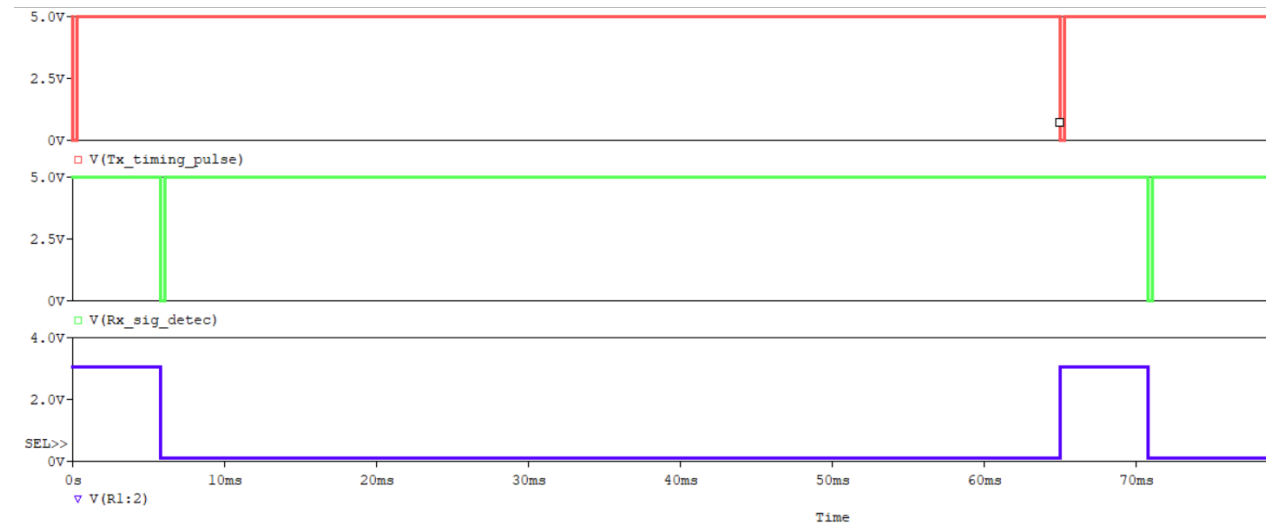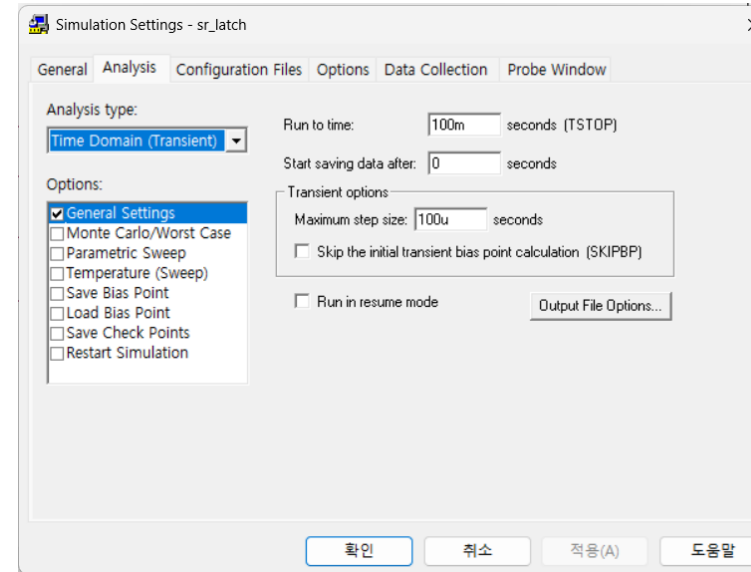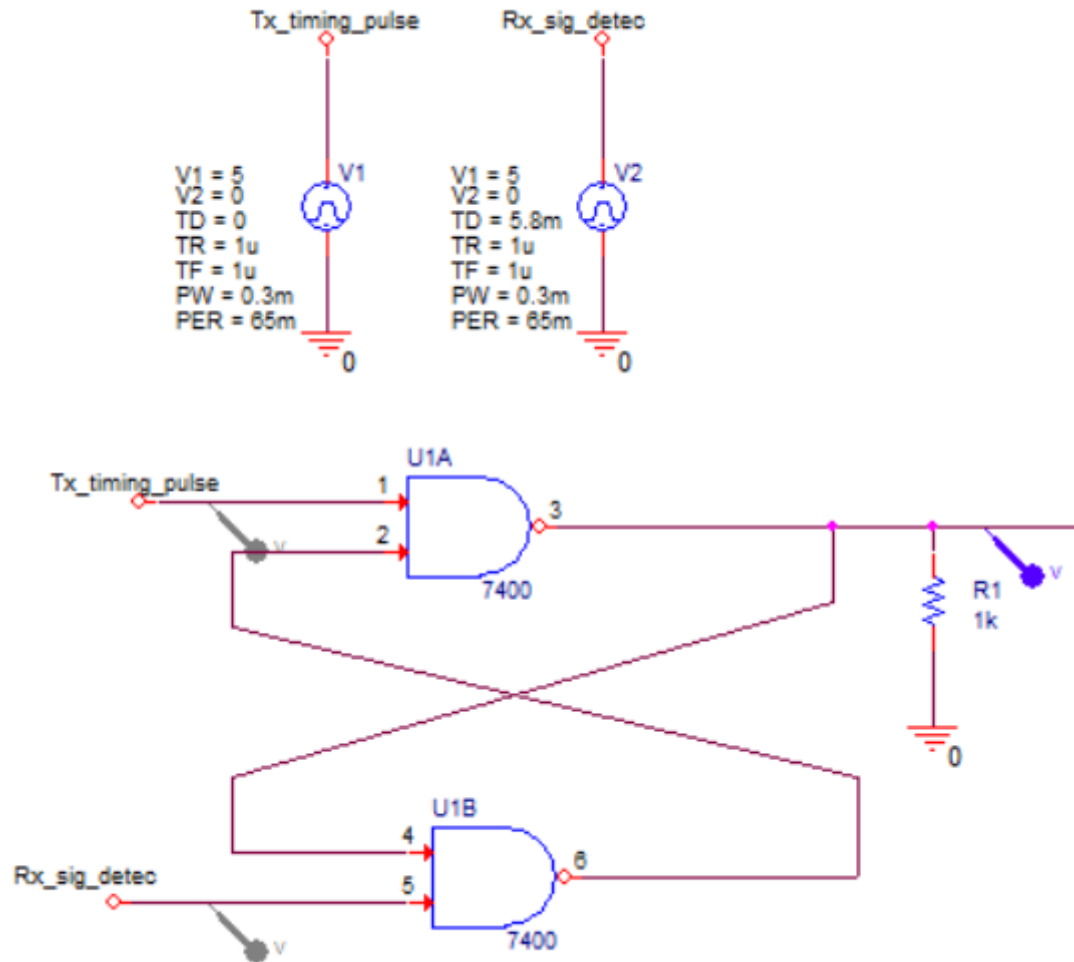





SR Latch High Output → Tx-Rx time interval

8. Counter Clock Generator

Block Purpose & Function




1. Generate 17.18 kHz clock pulses so that 1 m corresponds to 100 counts
2. Supply pulses only during the Tx–Rx timing gate interval

8. Counter Clock Generator

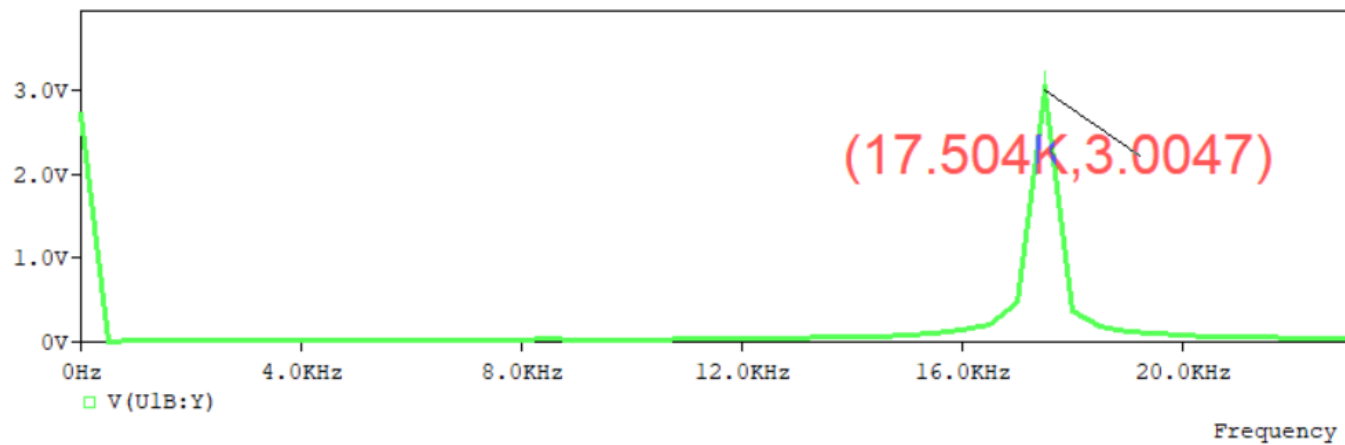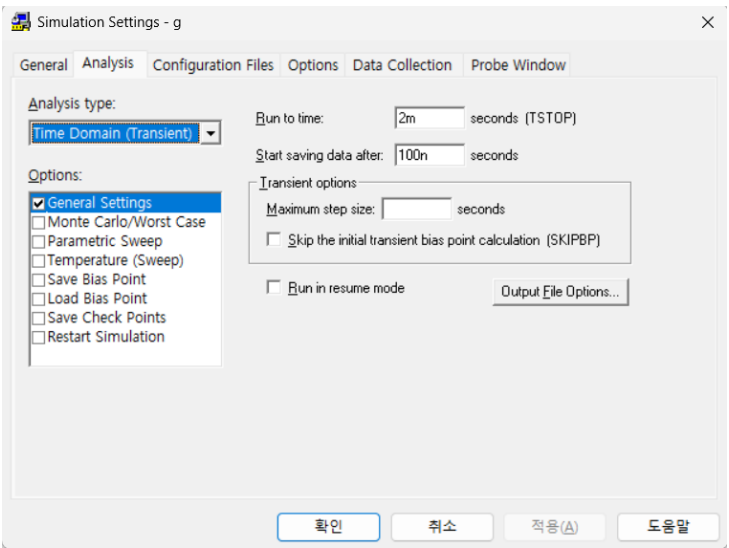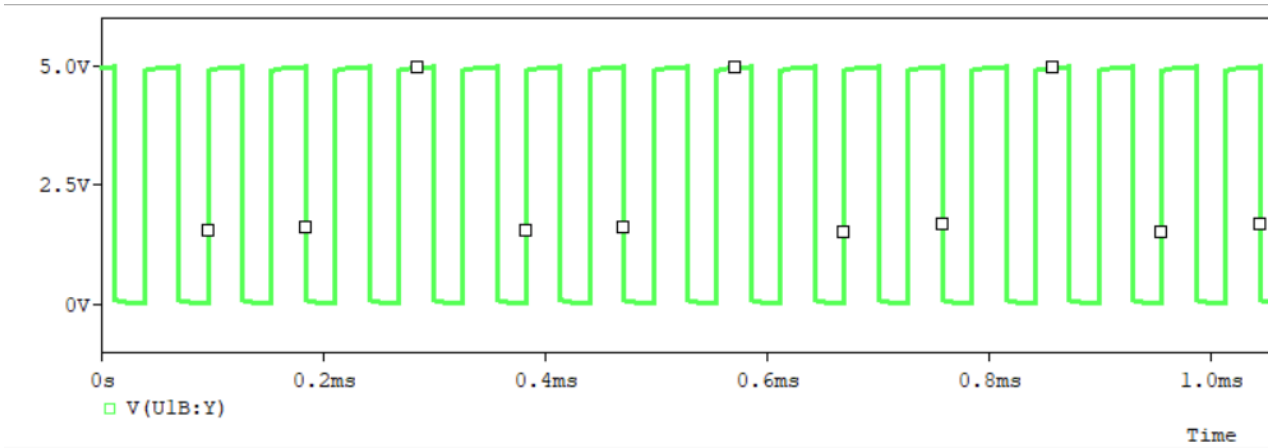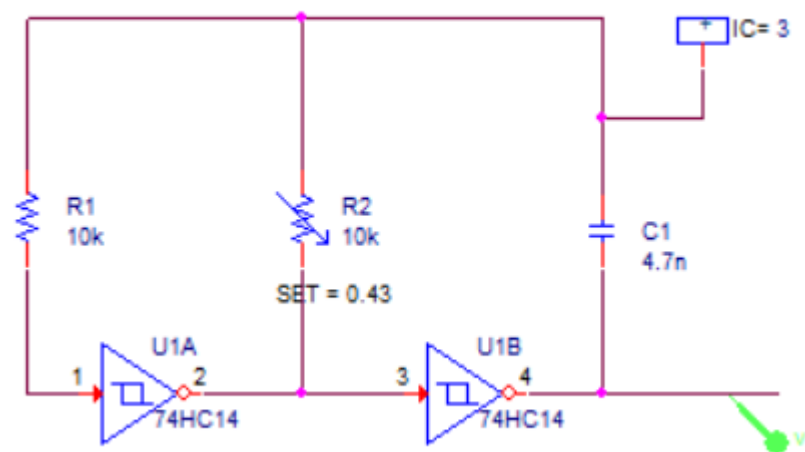

Design, Simulation & Measurements

8. Counter Clock Generator

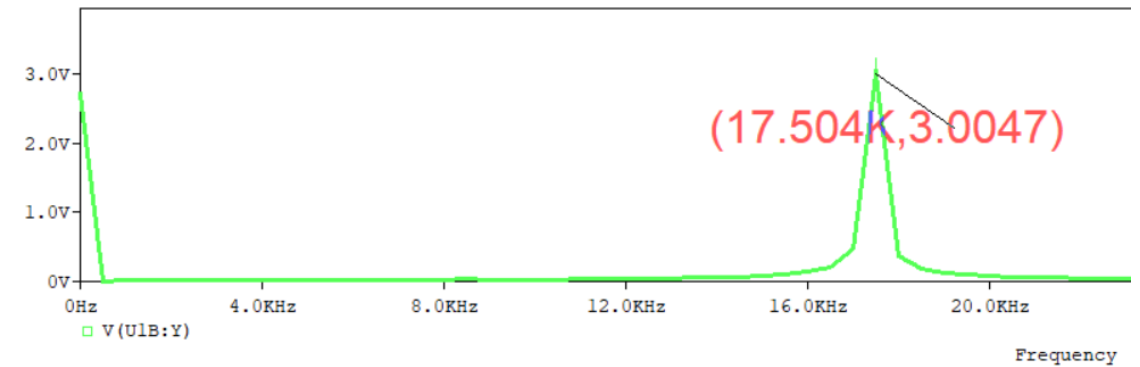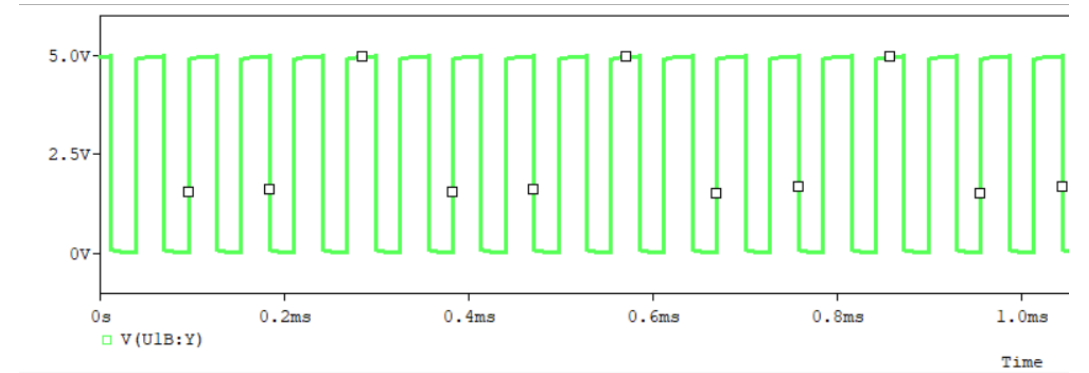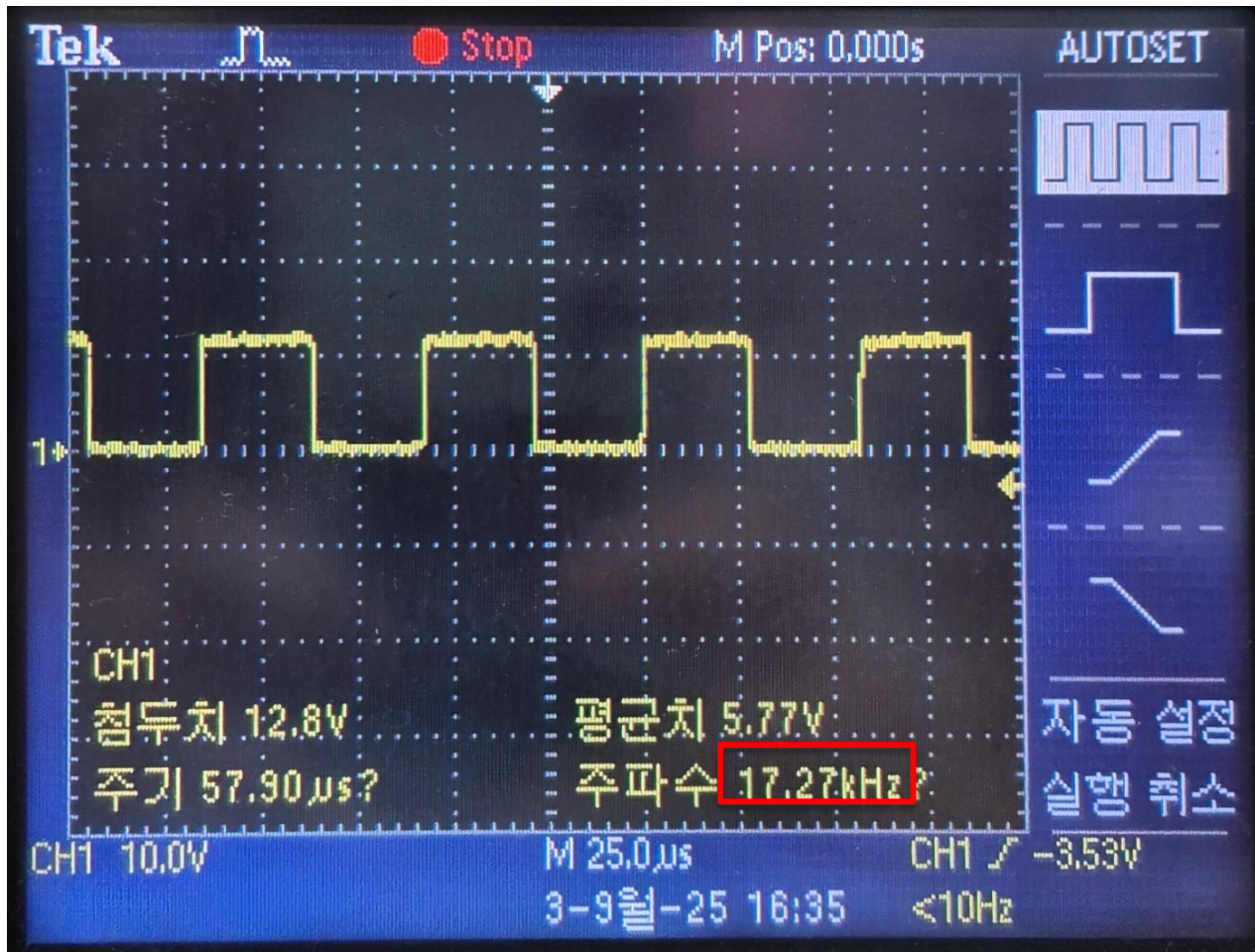




9. Counter Clear & Latch Clear Pulse Generator

Block Purpose & Function

1. Generate control pulses for counter operation during measurement
2. Provide a counter clear pulse at transmission (Tx) to reset counting
3. Provide a latch clear pulse at reception (Rx) to store the measured value


Design, Simulation & Measurements

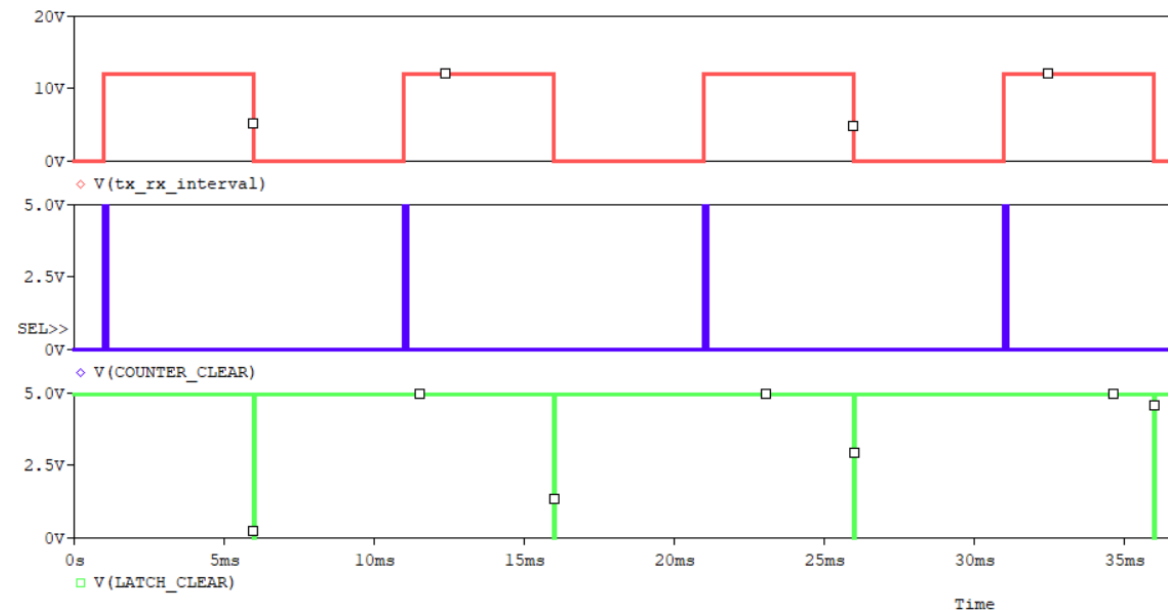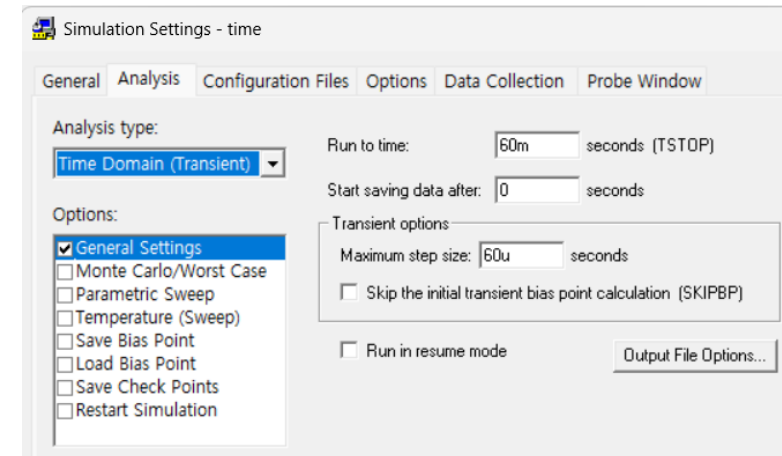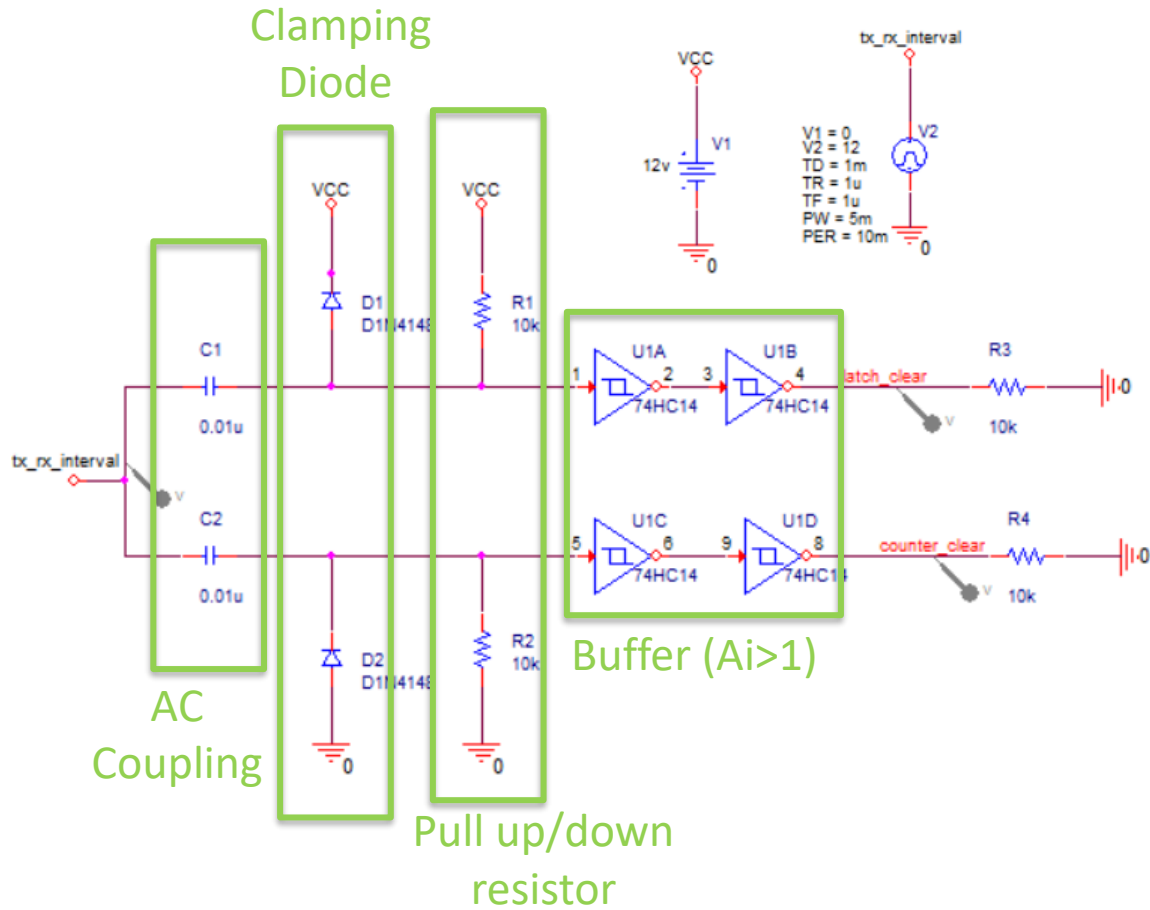9. Counter Clear & Latch Clear Pulse Generator




Design, Simulation & Measurements

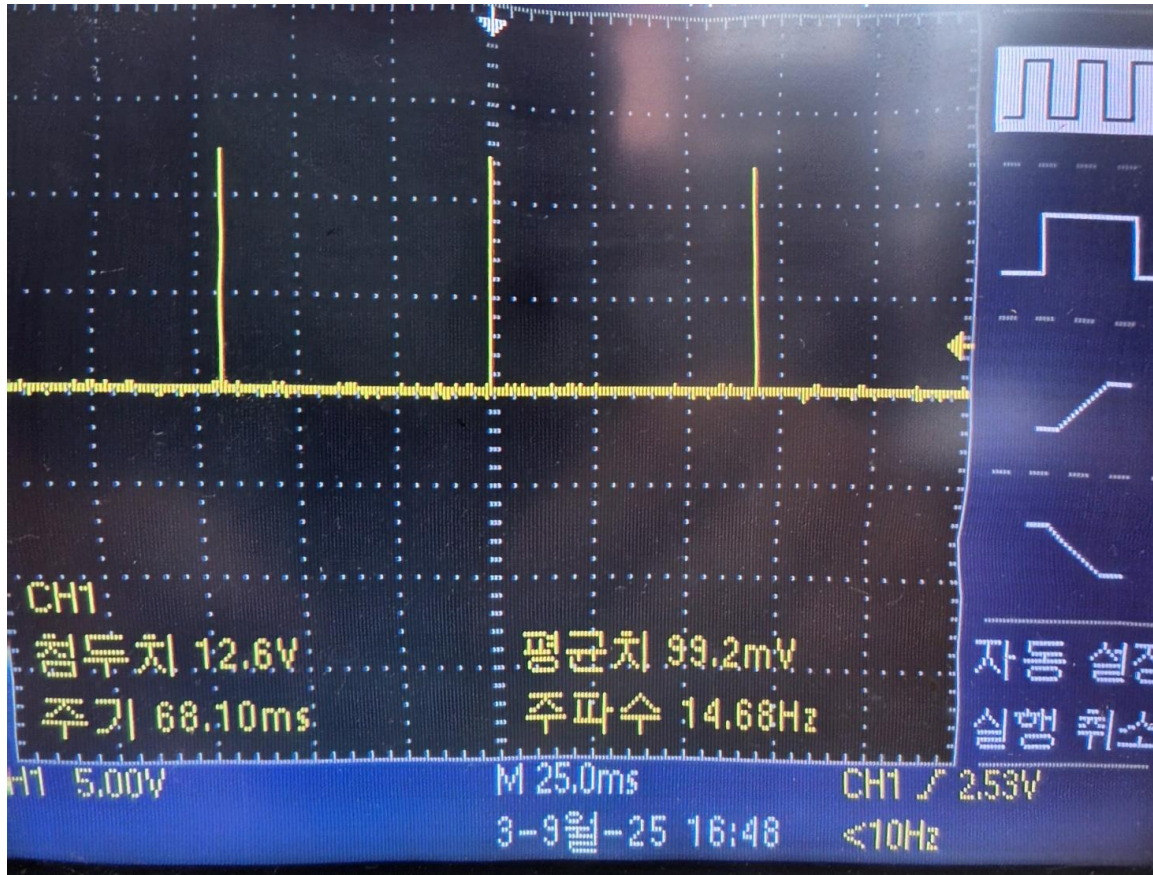9. Counter Clear & Latch Clear Pulse Generator



<Counter Clear Pulse>

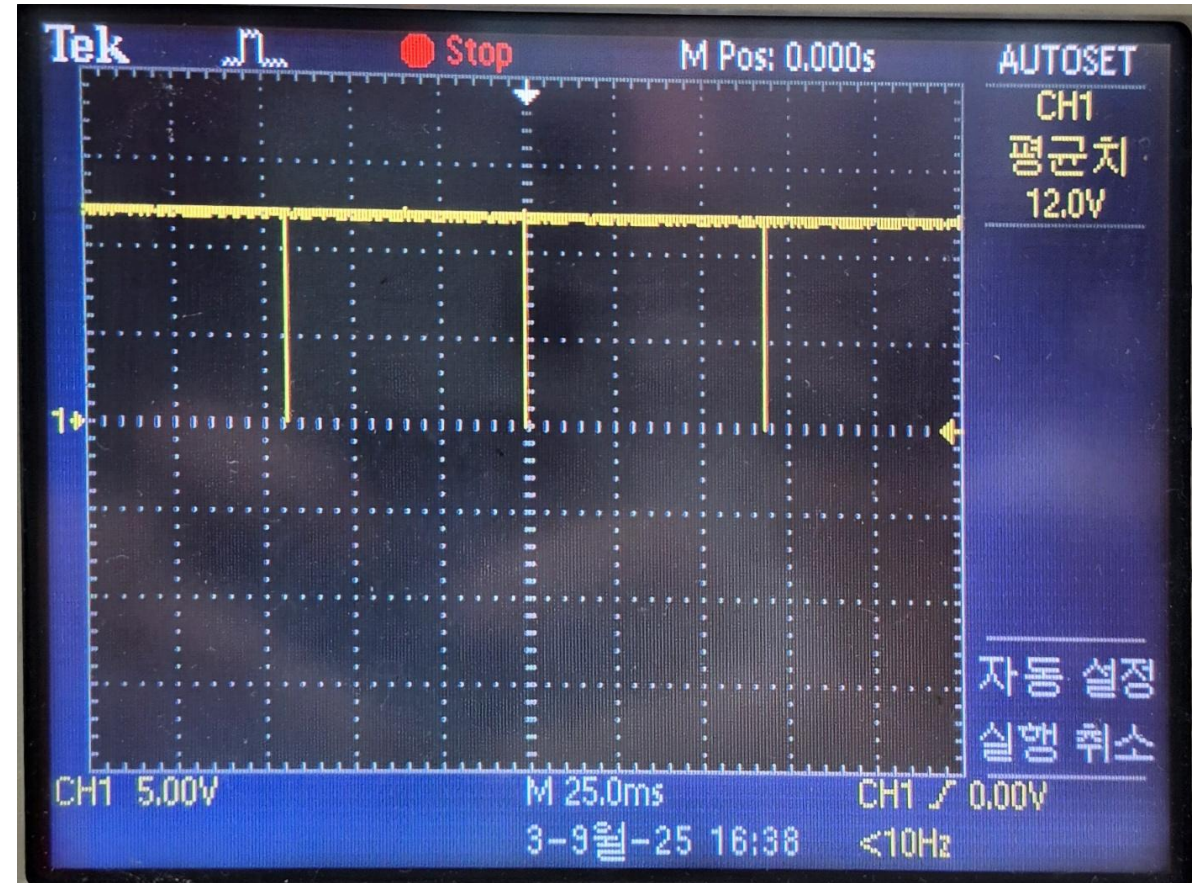

<Latch Clear Pulse>


10. Time Measurement Unit (Counter / Decoder) & 7-Segment Display Output (FND)

Block Purpose & Function

1. Count pulses during the Tx–Rx timing interval to calculate distance
2. Decode the count and display the measured distance on 7-Segment FND

Design, Simulation & Measurements

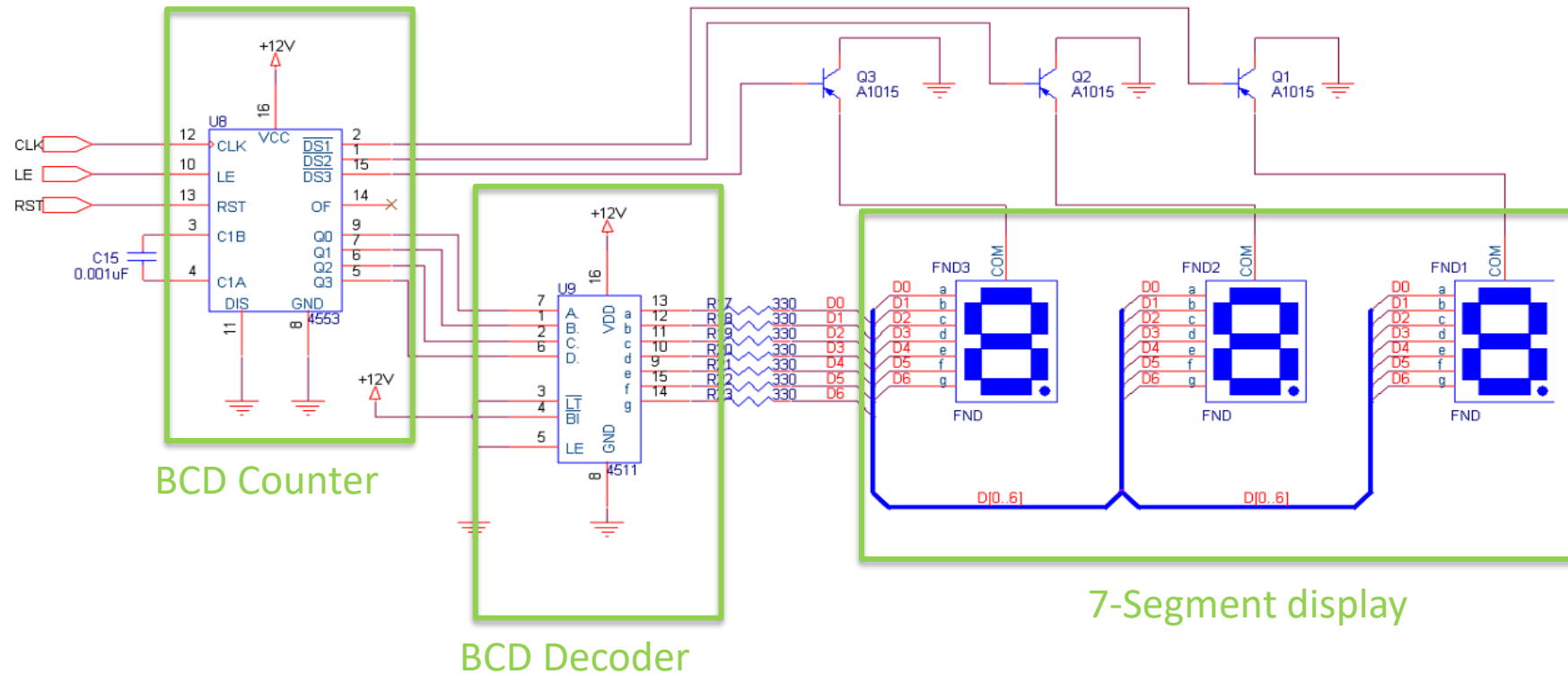10. Time Measurement Unit (Counter / Decoder) & 7-Segment Display Output (FND)





Count pulses during the Tx–Rx interval using a BCD counter.

Use a BCD decoder to convert the count into segment signals.

Drive the 7-Segment display (FND) to show the measured distance.

PCB & Demo photos

PCB Circuit Photo

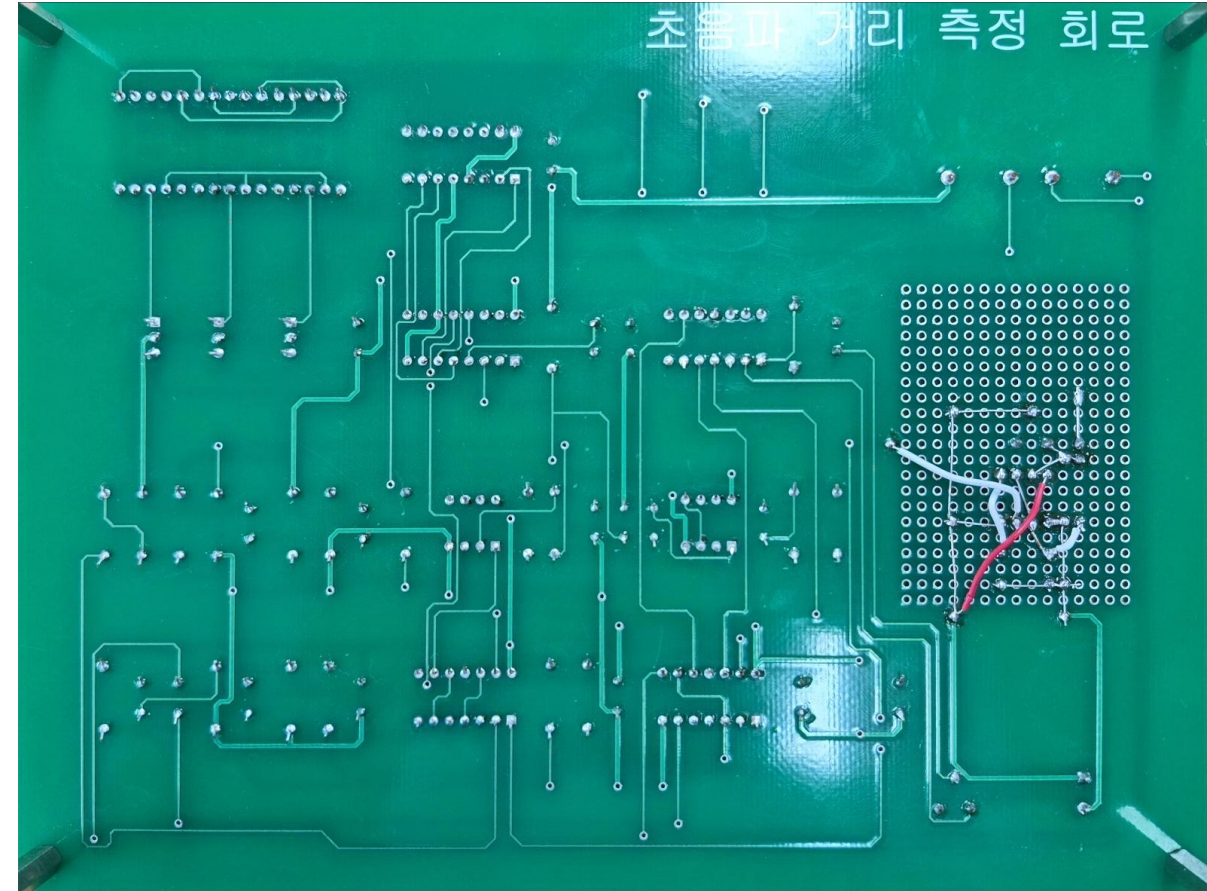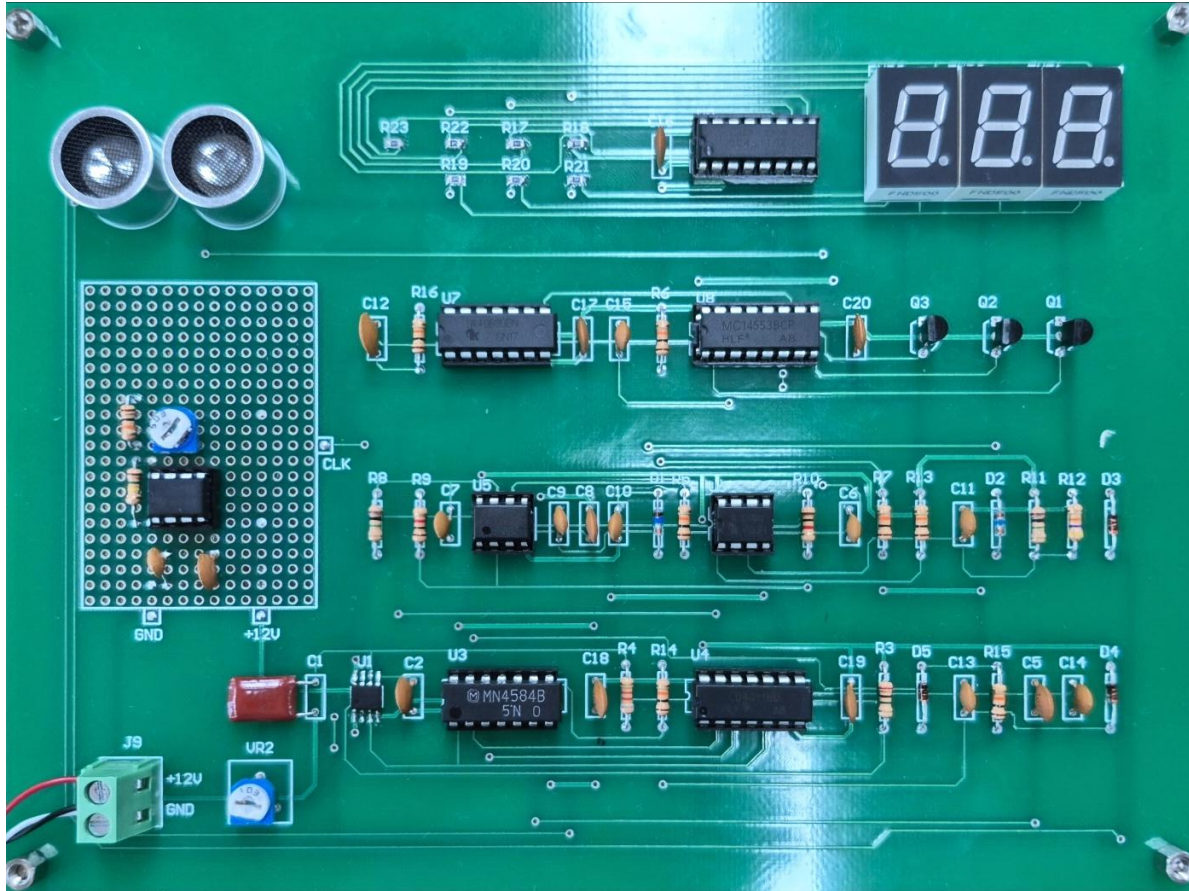

PCB & Demo photos

Demo Photos



Distance	30	50	70
Measurement result	30	51	70
Error	0	1	0

PCB & Demo photos

Demo Photos




Distance	90	110
Measurement result	90	112
Error	0	2

Issues & Improvements

- 1) OP-amp gain shortfall
- 2) No ESD protection on the supply I/O
- 3) Grounding problems (mixed/unstable GND)
- 4) Metastability (async control vs. clock)
- 5) No resistors on FND drivers
- 6) NE555 RC Oscillator — Temperature Drift
- 7) Low flexibility/expandability

Issues & Improvements

1. OP-amp gain shortfall

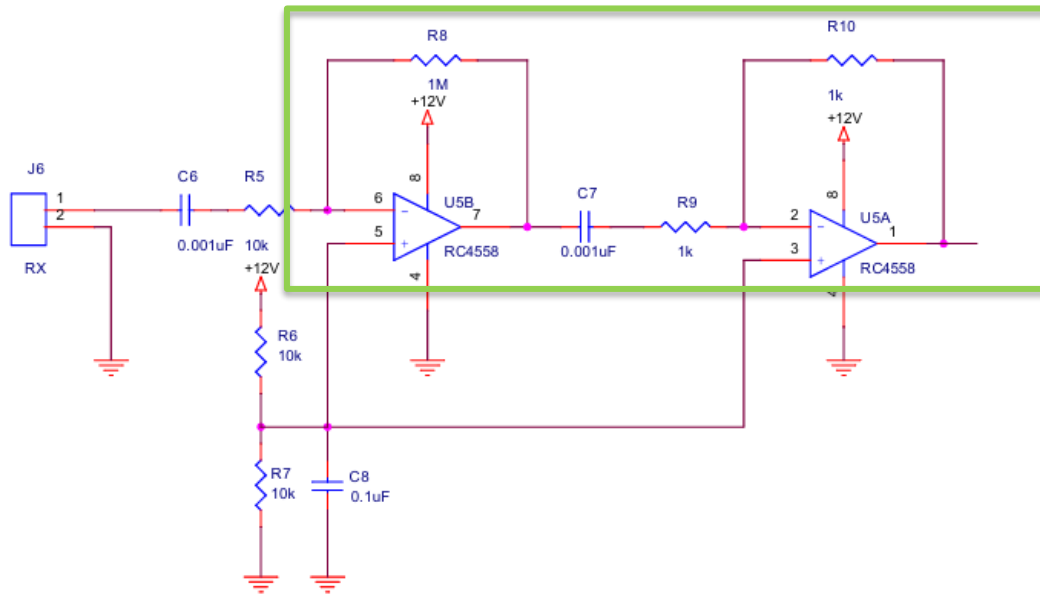

Issue :


Gain = $GBW / BW = 3 \text{ MHz} / 40 \text{ kHz} \approx 75 \rightarrow 100\times$ gain is not achievable (in one stage).

Improvement :

Reconfigure to $[\times 10] + [\times 10]$ two-stage op-amp $\rightarrow$ overall $\times 100$ gain achievable (stable).

Issues & Improvements

2. No ESD protection on the supply I/O

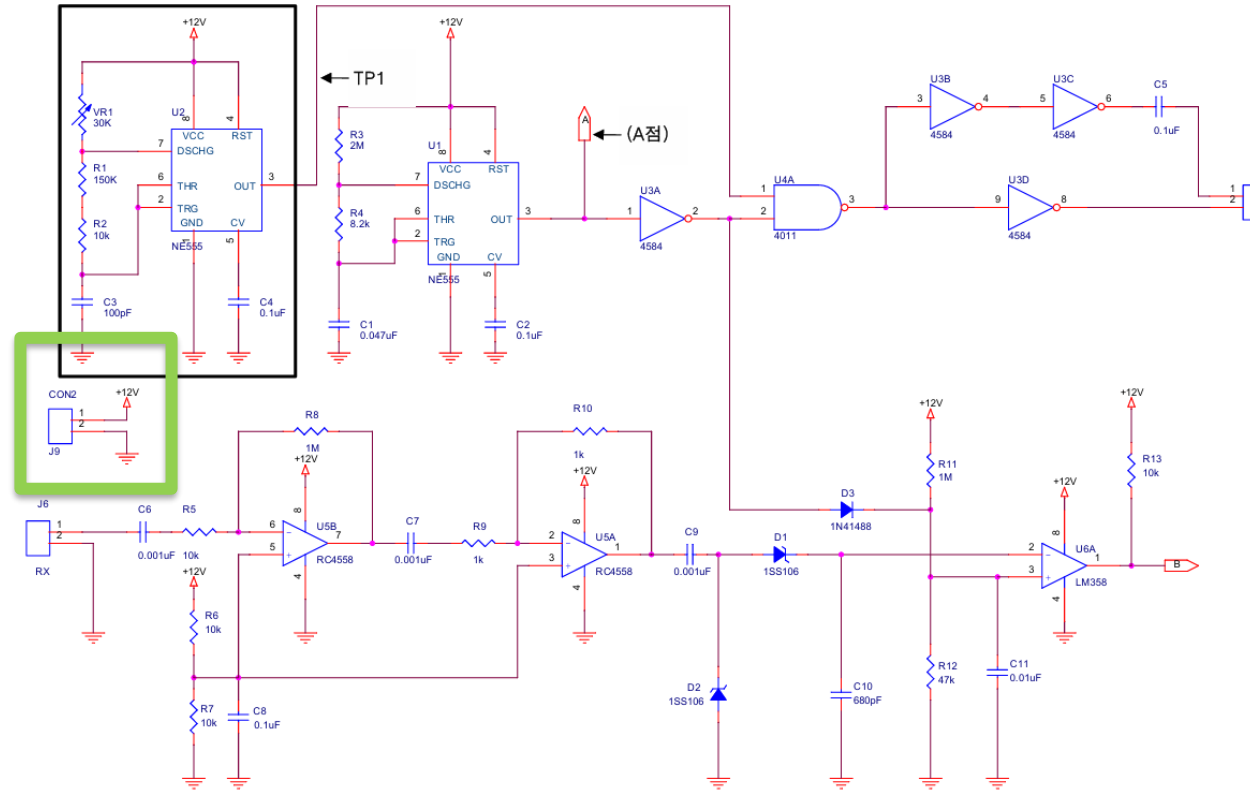

Issue:


- **Surges/ESD** can stress or damage the circuit.

Improvement :

- Add **TVS** diodes at supply inputs and external connectors (series R / ferrite as needed).

Issues & Improvements

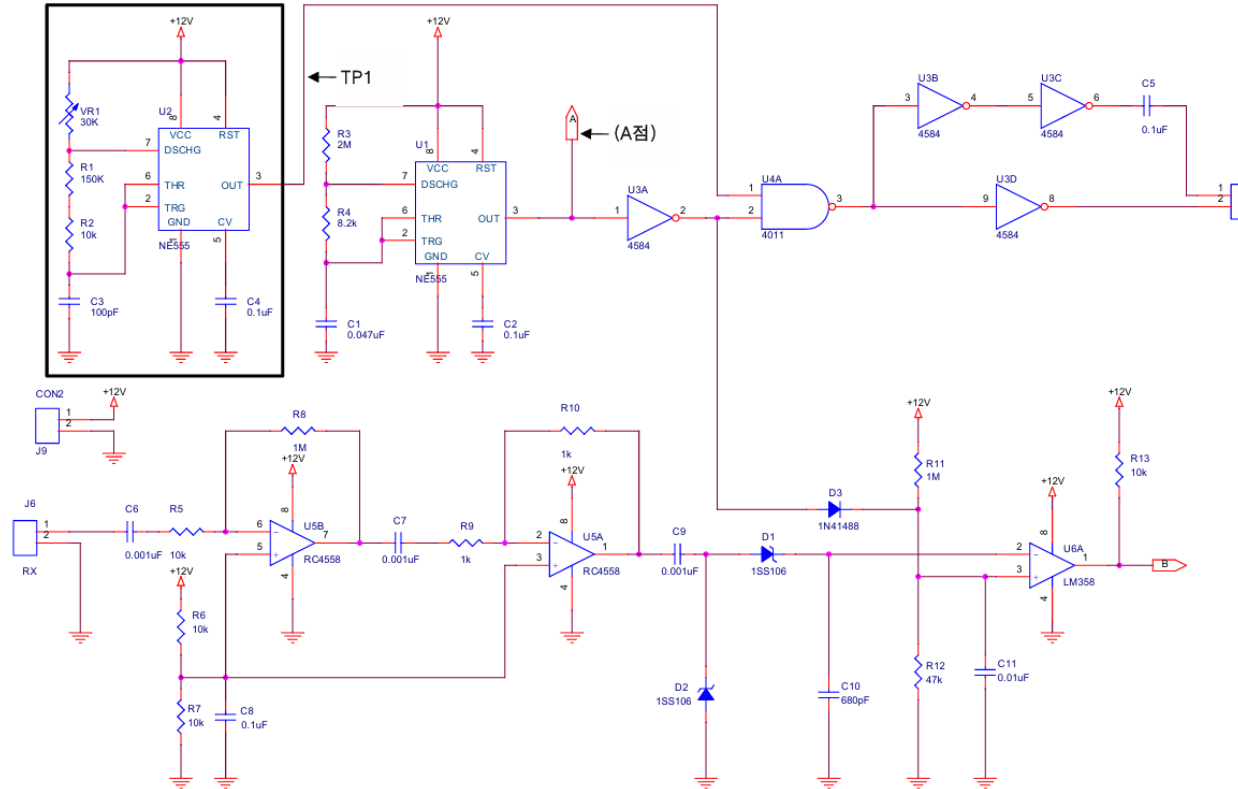3. Grounding problems (mixed/unstable GND)



Issue:


- Power and signal grounds are not separated → noise coupling, unstable reference. EMI increase

Improvements:

- Split power vs. signal GND, use ferrite beads + decoupling caps, and a copper ground pour .

Issues & Improvements

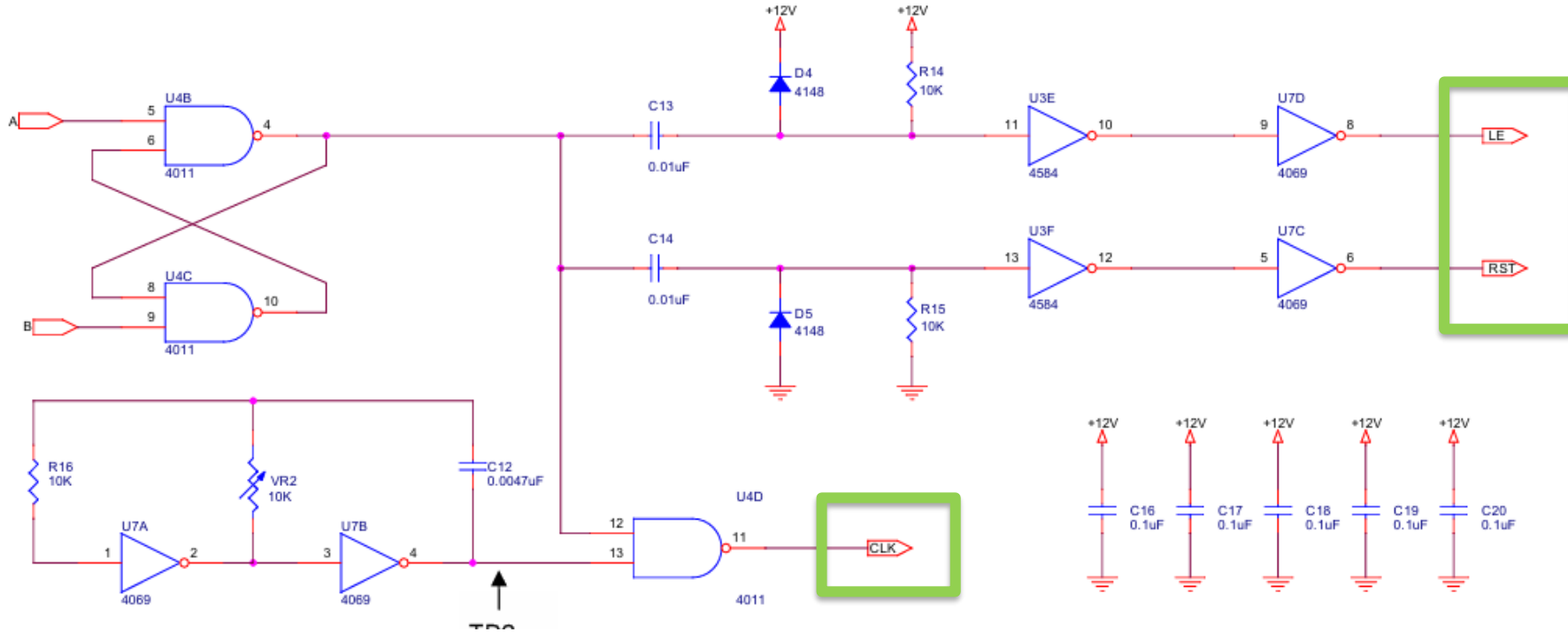4. Metastability Problem (async control vs. clock)



Issue:


- Control signals and the counter clock are not synchronized → wrong counts.

Improvements:

- Synchronize with 2-FF synchronizers** and use a synchronous clock
- option: **172 kHz clock** for 0.1-cm resolution,
- Use an **MCU** to synchronize the gate/clock and average multiple readings (output the mode).

Issues & Improvements

5. No resistors on FND drivers

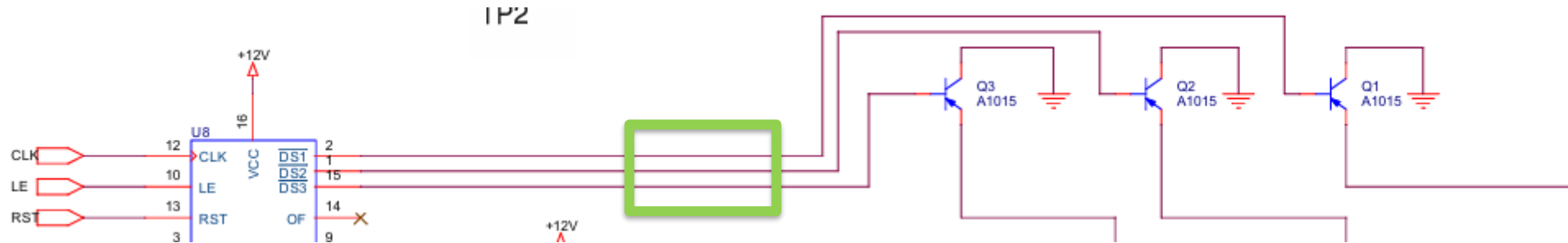


Issue:

- Missing base series and pull resistors → stress, reduced lifetime/ghosting.
- Add **series base resistors** and proper pull-up/pull-down; limit segment current.

Issues & Improvements

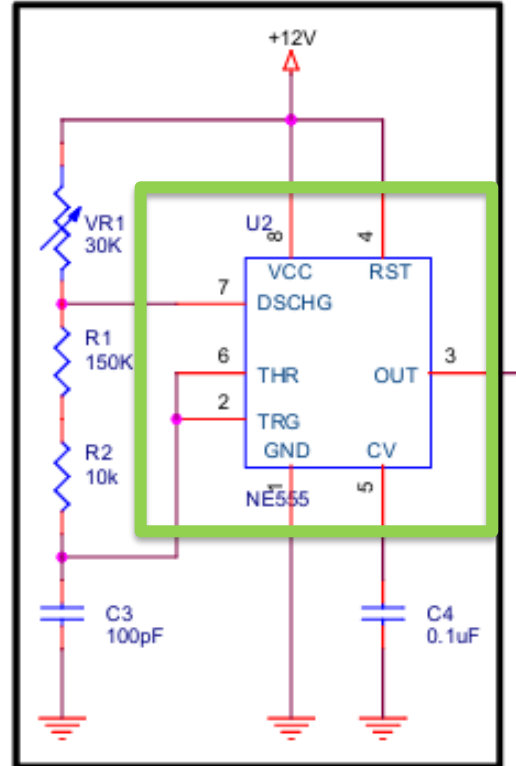6. NE555 RC Oscillator — Temperature Drift



Issue:


- The NE555-based RC oscillator shows significant frequency shift with temperature (40 kHz varies).

Improvement:

- Use a **crystal oscillator** (or TCXO) for stable frequency.

Issues & Improvements

7. Low flexibility/expandability

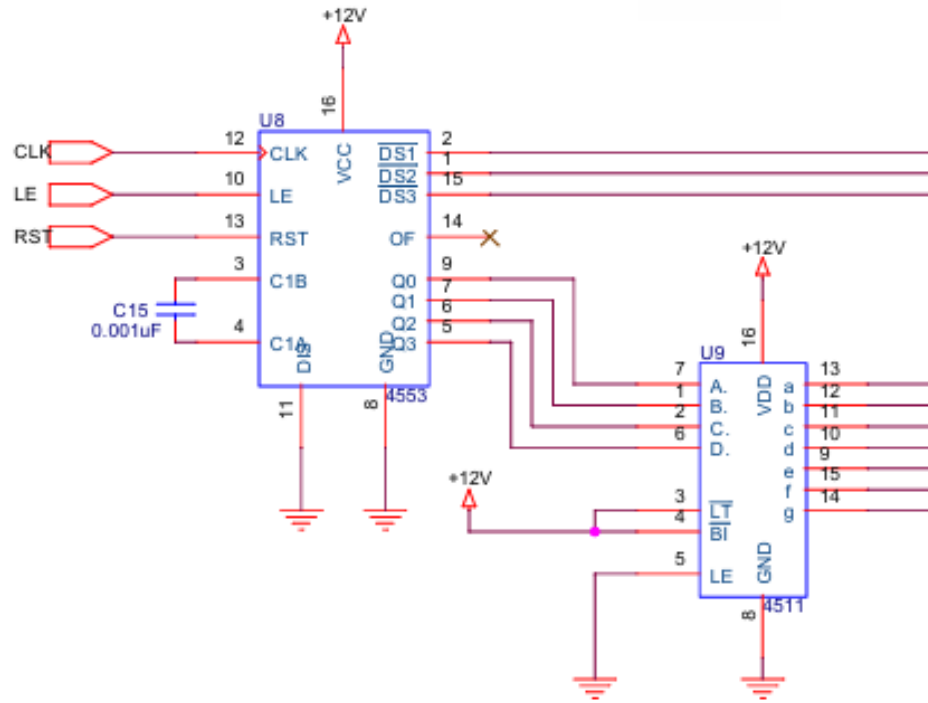

Issue:

- Hard to change features with discrete logic only.

Improvements:

- Use a low-cost **MCU** to integrate timing, gating, counting, filtering, and display; firmware calibration and synchronized clocks.

CONTACT



E-mail

emh0412@naver.com



Mobile

+82 10 6616 2655